

6. (5 pts) Design a single-bit full adder using 2 4-input Muxes. (A 4-input Mux has 4 data inputs and 2 control lines).

7. (5 pts) Assume you have 8-bit data words, and your memory system supports Single Error Correction. For each of the following patterns received from memory identify and correct any errors that may have occurred during transmission or storage. The first one is done for you.

Given: **1 0 1 0 0 1 0 0 0 1 1 0**

The Data Word is: **10101001**

Given: **1 0 0 0 0 0 0 0 0 0 0 0**

The Data Word is:

8. (25pts) Given the following state transition table, draw the Karnaugh maps for $Y1'$, $Y2'$, and $Y3'$, and Z in terms of X , $Y1$, $Y2$ and $Y3$, and then write minimum boolean equations for each.

Present State			Next State						Output (Z)	
Y1	Y2	Y3	X=0			X=1			X=0	X=1
			Y1'	Y2'	Y3'	Y1'	Y2'	Y3'		
0	0	0	0	0	0	0	0	1	0	0
0	0	1	0	1	0	0	1	1	0	1
0	1	0	1	0	0	1	0	1	0	0
0	1	1	1	1	1	1	0	0	0	1
1	0	0	0	0	1	0	1	0	1	0
1	0	1	0	1	1	0	1	0	0	1
1	1	1	1	0	1	1	1	1	0	1

9. (20pts) Given the following Karnaugh maps, implement the sequential machine using a JK FF for Y1, a RS FF for Y2, and a Toggle FF for Y3. You do not need to draw the gates, but you do need to write down the input equations for each of the inputs of each of the Flip Flops in the circuit.

Y1'

		X		
	1			1
		1	1	
		1	1	
Y2	1			1
		Y1		

Y2'

		X		
	1			1
		1	1	d
	1	d		1
Y2		1	1	
		Y1		

Y3'

		X		
	d			
	1	d	1	1
			d	
Y2	1	1	1	1
		Y1		

10. (30 pts) A vending machine takes nickels, dimes and quarters. Pop is to be dispensed when a total of 30 cents has been deposited. Only one coin can be deposited at a time. Let $X_1=25$ cents, $X_2=10$ cents, and $X_3=5$ cents. Draw the State Transition Diagram (the circles and the arcs) for this finite state machine. Let S_0 =nothing deposited (the Start state). Once you have a state transition diagram, assign bit patterns to each state and write down the corresponding state transition table. Assume you are using a Mealy model. Also, label the transitions on the diagram using the following format:

$$\frac{X_1 X_2 X_3}{Z}$$

So, for example,

$$\frac{1 0 0}{0}$$

would be used to indicate that a quarter was deposited, and the output at that point should be a 0.