
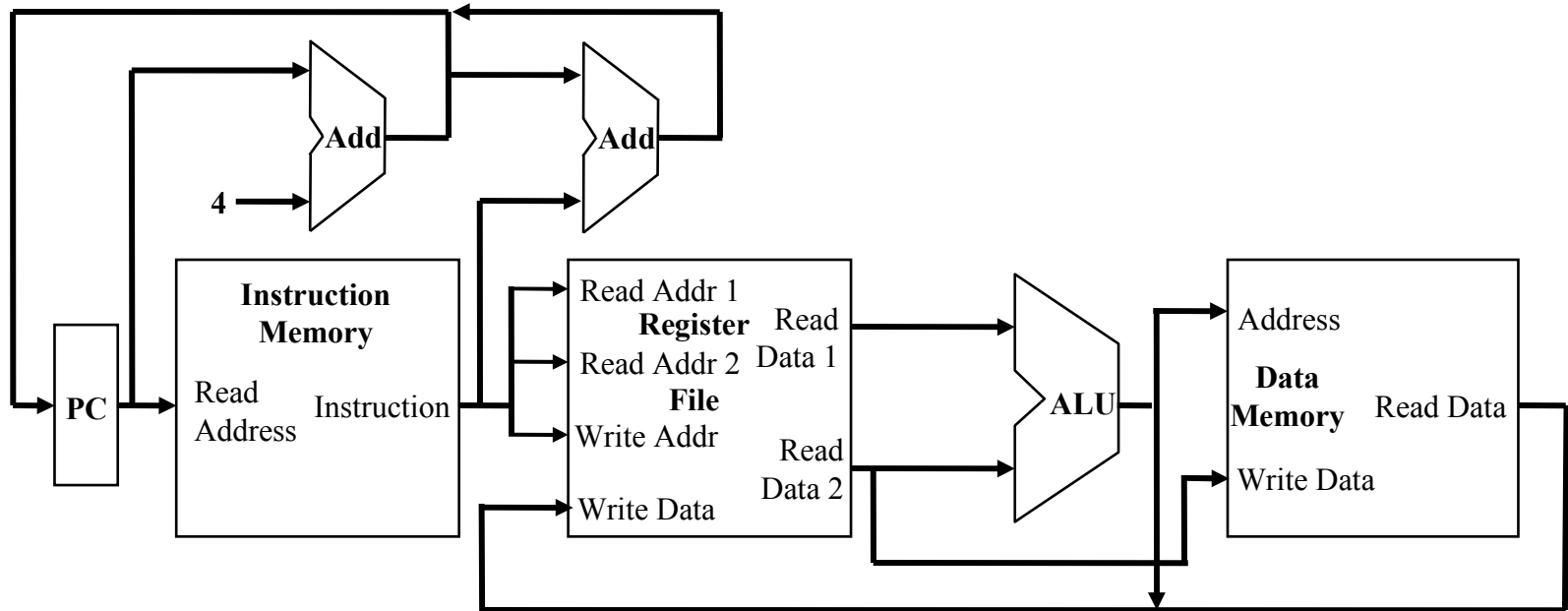


The Processor: Overview

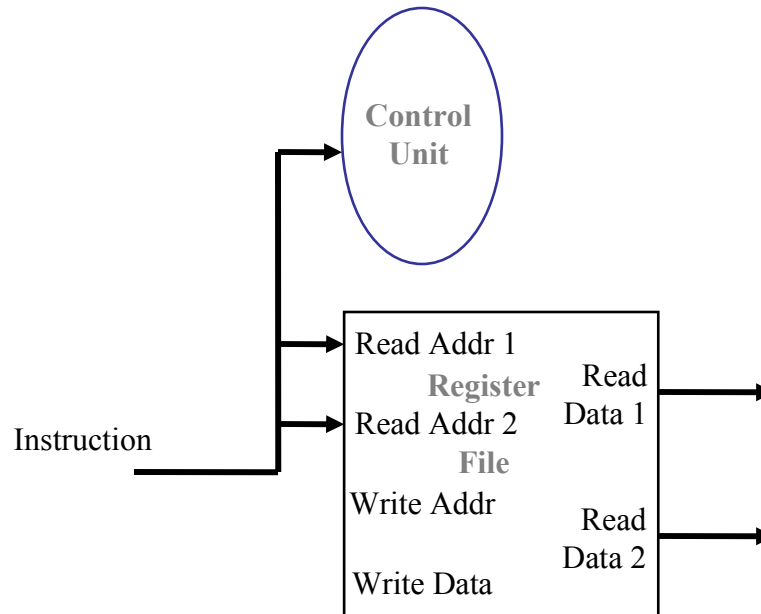

Decoding Instructions


- Decoding instructions involves
 - Sending the instruction's fields to the control unit



- Reading two values from the Register File
 - Register File addresses are contained in the instruction

Executing R-Type Instructions

 
- R-type instructions (**add**, **sub**, **slt**, **and**, **or**)
 - Perform the operation on values in rs and rt
 - Store the result back into the Register File (rd)



- The Register File is not written every cycle, so we need an explicit write control signal for the Register File


Executing Load and Store Operations

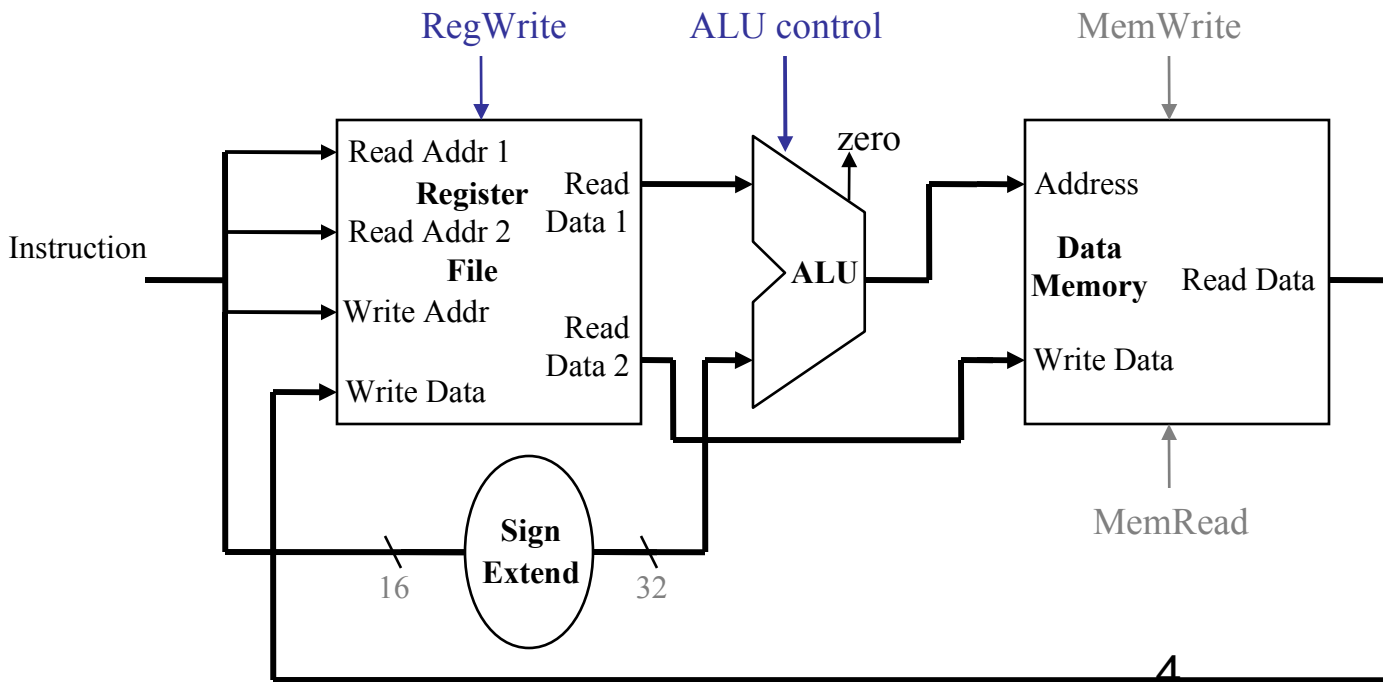- Load and store operations involve
 - Compute memory address (base register plus the 16-bit signed-extended offset field in the instruction)
 - **Store** value to the Data Memory
 - **Load** value to the Register File




Executing Branch Operations

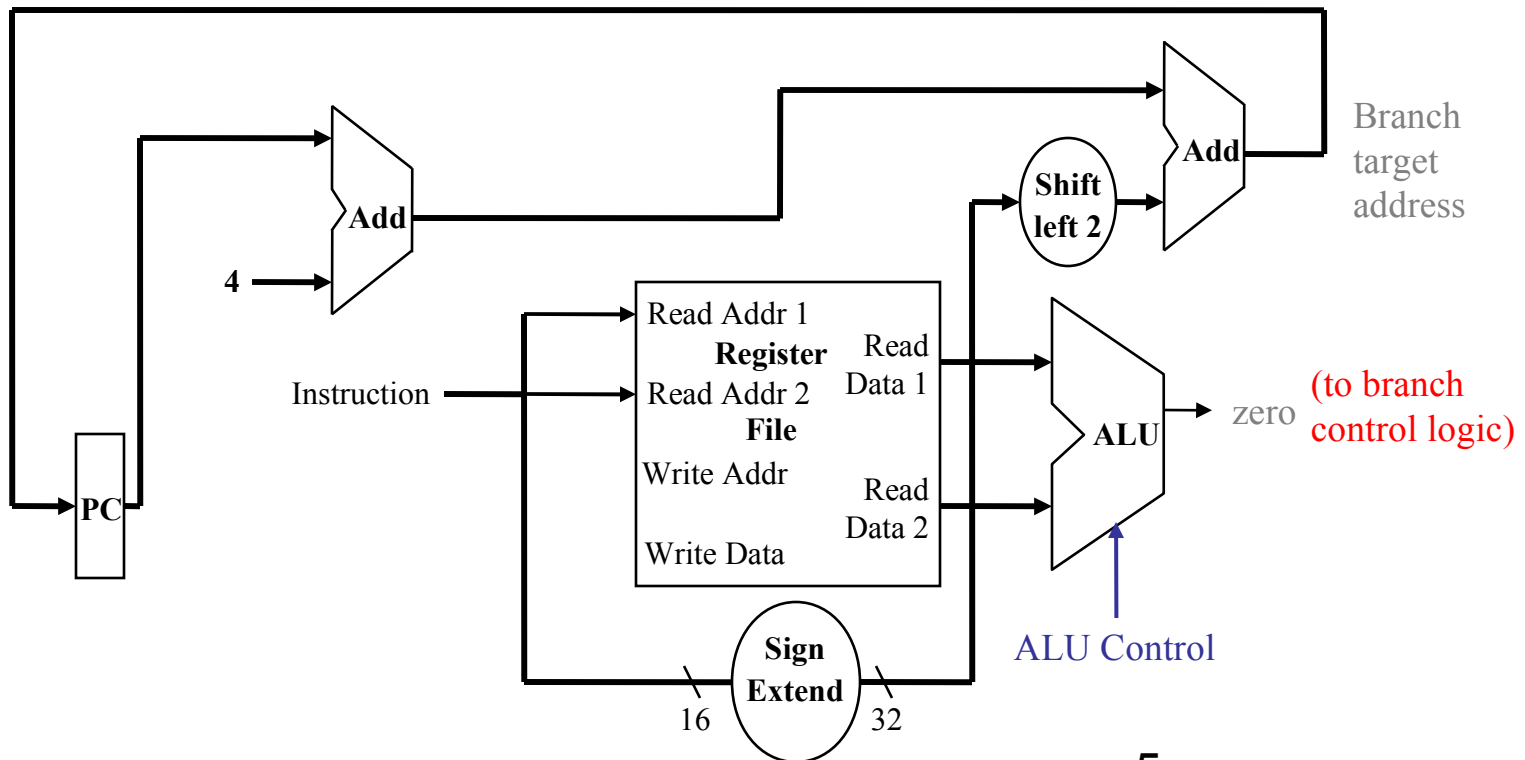- Branch operations involve
 - Compare the operands for equality (**zero**)
 - Compute the branch target address (PC plus the 16-bit signed-extended offset field in the instruction)



Executing Jump Operations

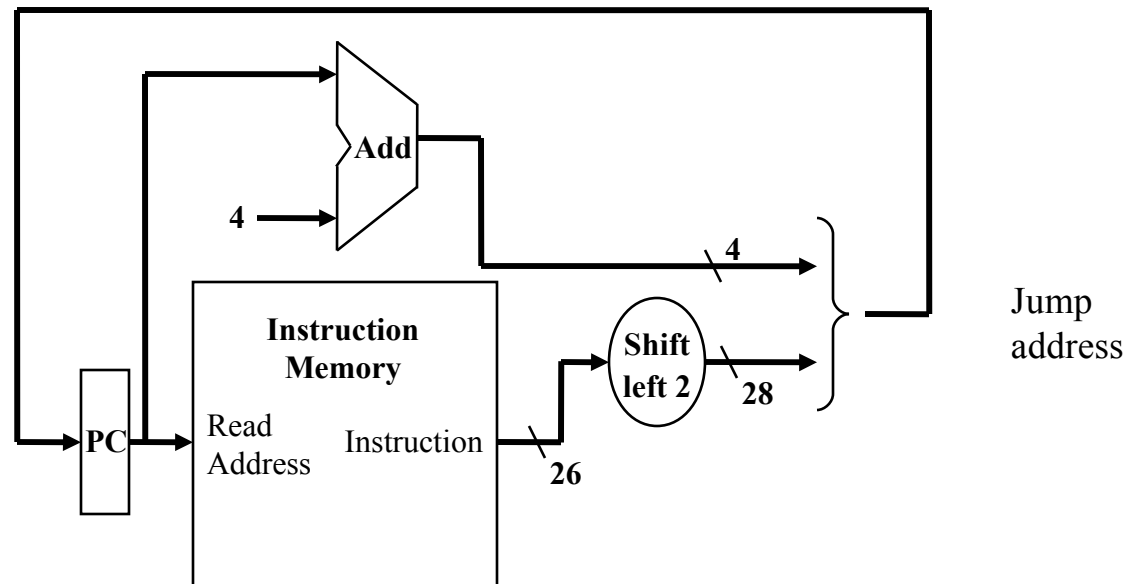
- Jump operation involves
 - Replace the lower 28 bits of the PC with the lower 26 bits of the instruction shifted left by 2 bits



Creating a Single Datapath


- Assemble the datapath segments and add control lines and multiplexers as needed
- Single cycle design – fetch, decode and execute each instructions in one clock cycle
 - No resource can be used more than once per instruction
 - Separate Instruction Memory and Data Memory
 - Multiple, parallel adders
 - Multiplexers needed at the input of shared elements
 - Write control signals for the Register File and Data Memory
- Cycle time is determined by length of the longest path
 - The “critical path”

The Complete Datapath

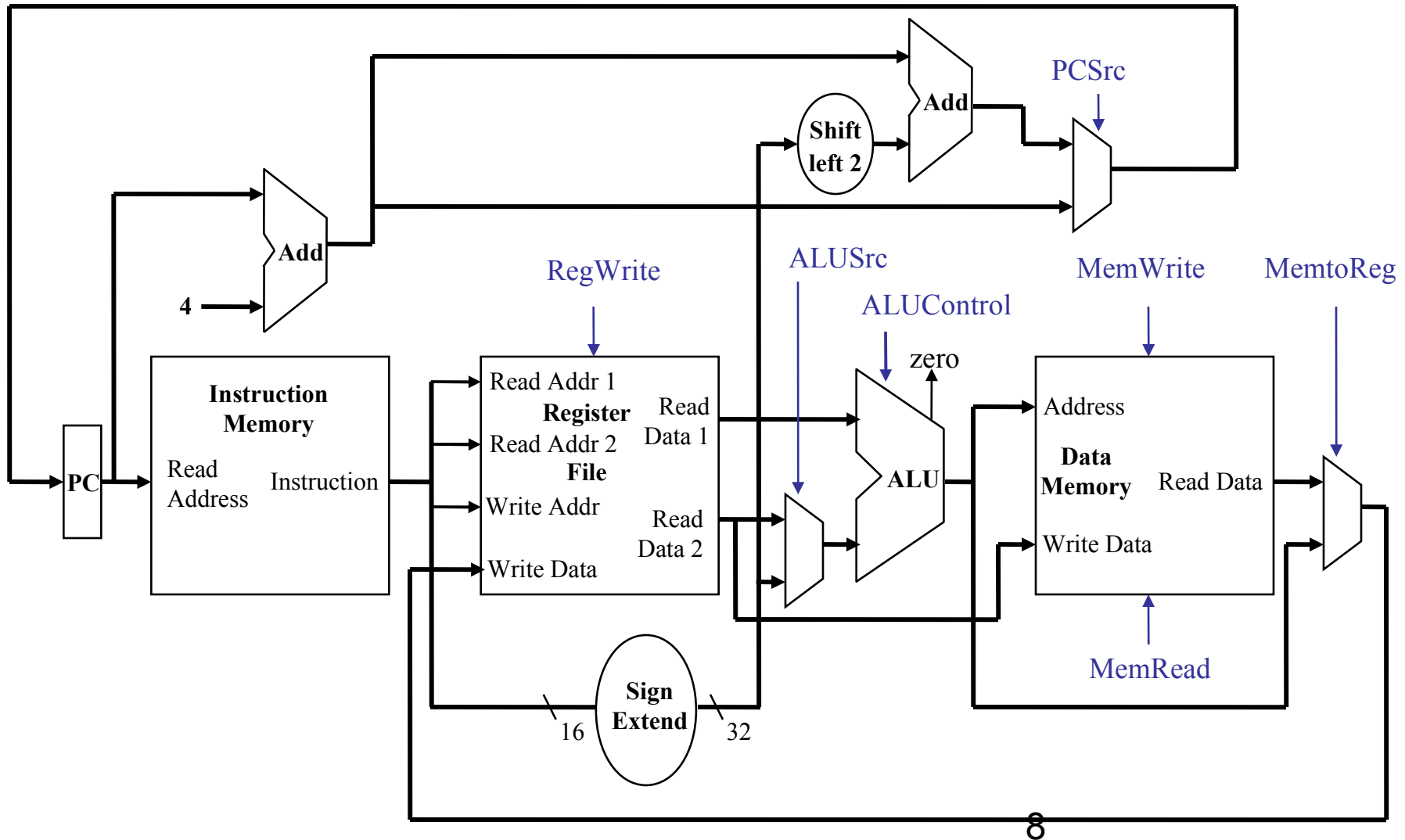

The Processor: Datapath & Control


- Our implementation of the MIPS is simplified
 - Memory-reference instructions: **lw**, **sw**
 - Arithmetic/Logical instructions: **add**, **sub**, **and**, **or**, **slt**
 - Control flow instructions: **beq**, **j**
- Generic implementation
 - Use the program counter (PC) to supply instruction address and fetch the from memory (and update the PC)
 - Decode the instruction (and read registers)
 - Execute the instruction
- All instructions (except **j**) use the ALU

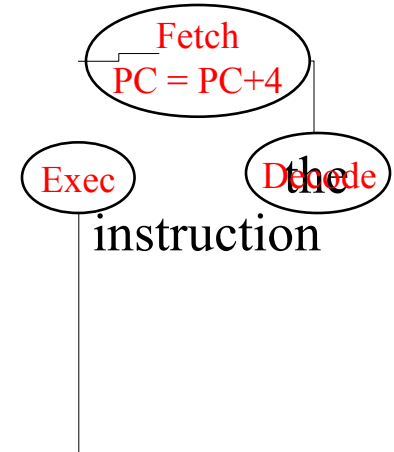


Adding the Control

- Selecting the operations to perform (ALU, Register File and Memory read/write)
- Controlling the flow of data (multiplexer inputs)
- Observations
 - op field **always** in bits 31-26
 - Address of registers to be read are **always** specified by the rs field (bits 25-21) and rt field (bits 20-16)
 - Address of register to be written is in one of **two** places
 - rt (bits 20-16) for I-type instructions
 - rd (bits 15-11) for R-type instructions
 - Offset for beq, lw, and sw **always** in bits 15-0


Single Cycle Datapath and Control

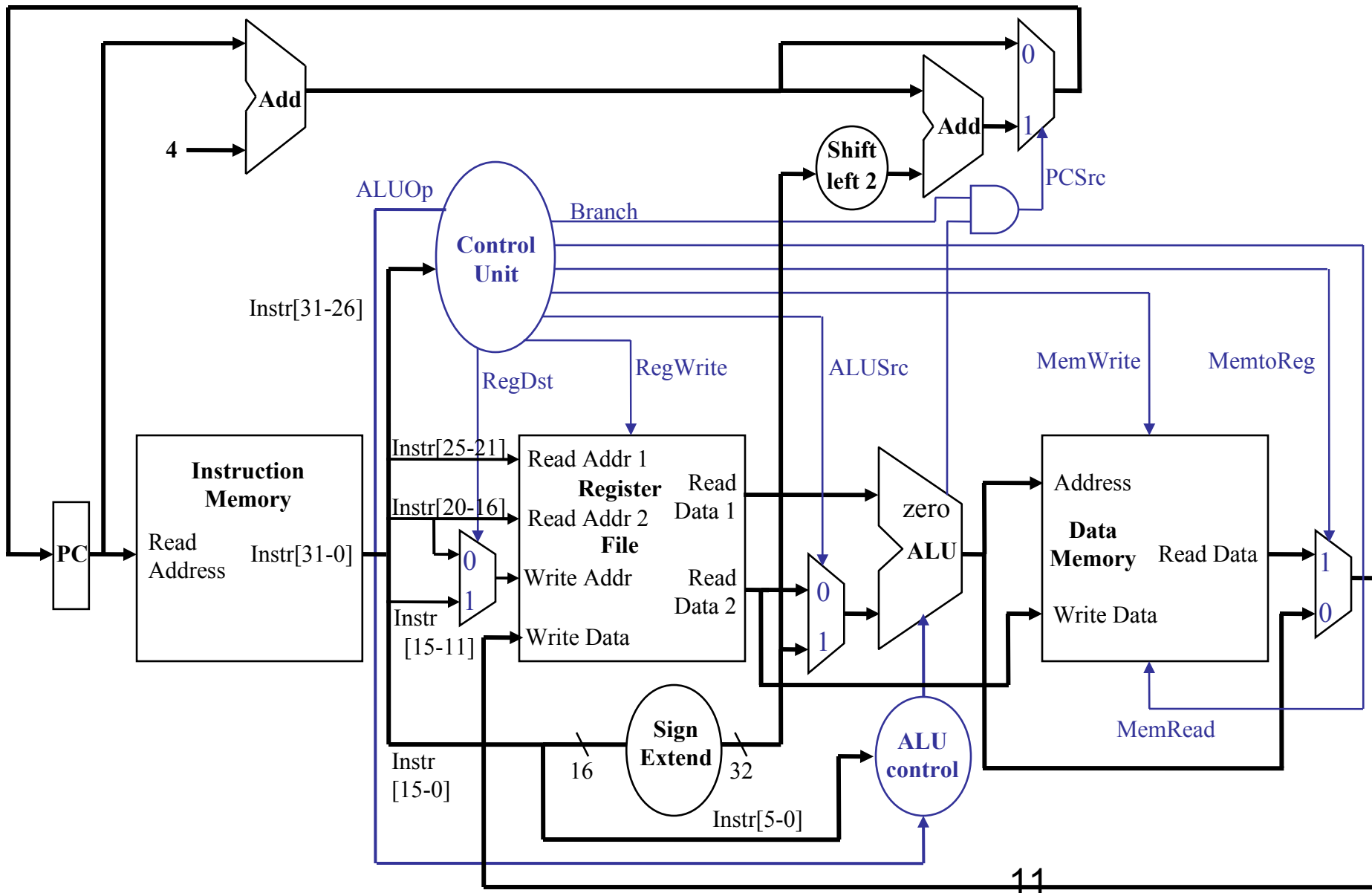


R-Type Instructions

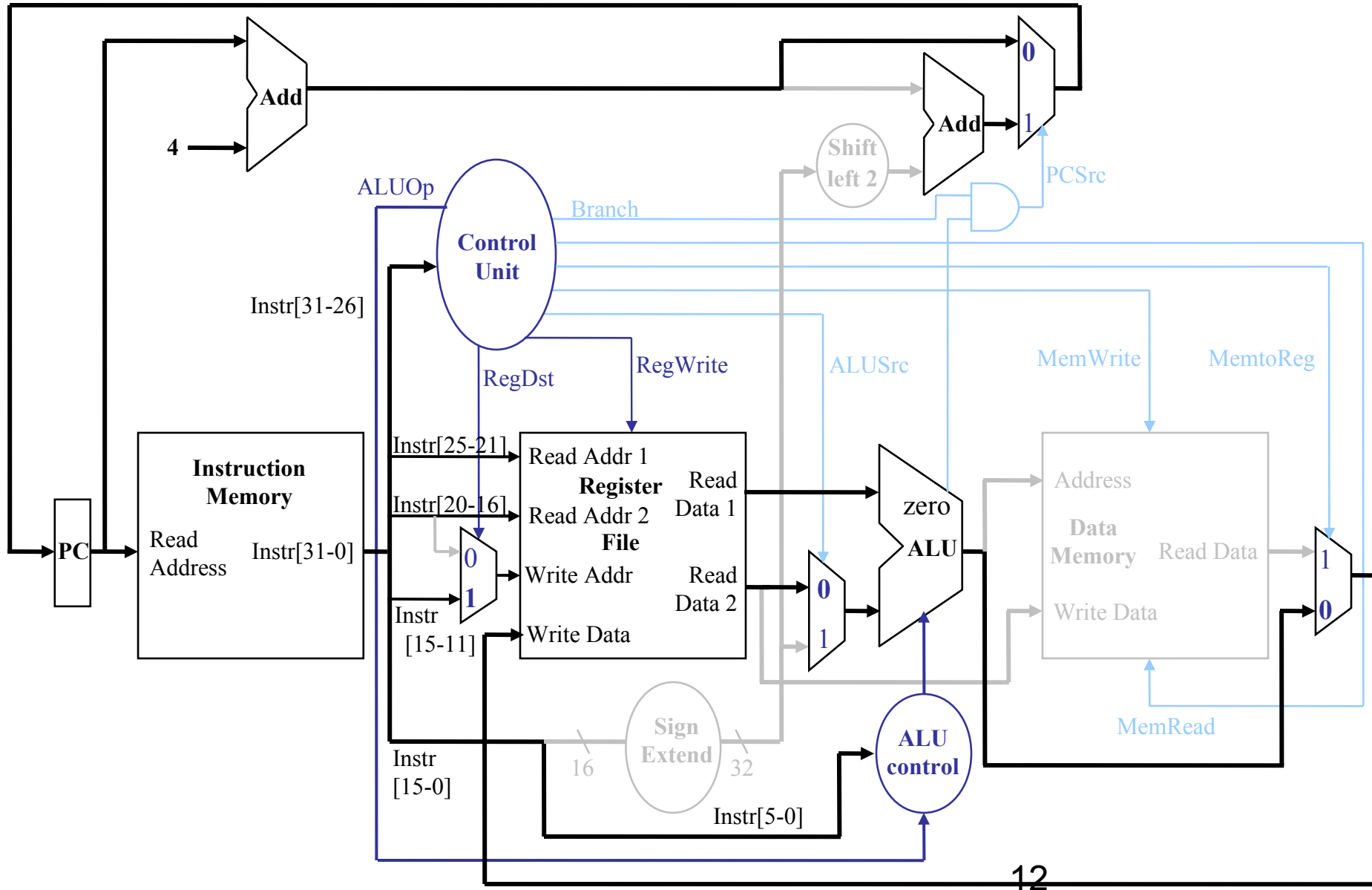

Load Instructions

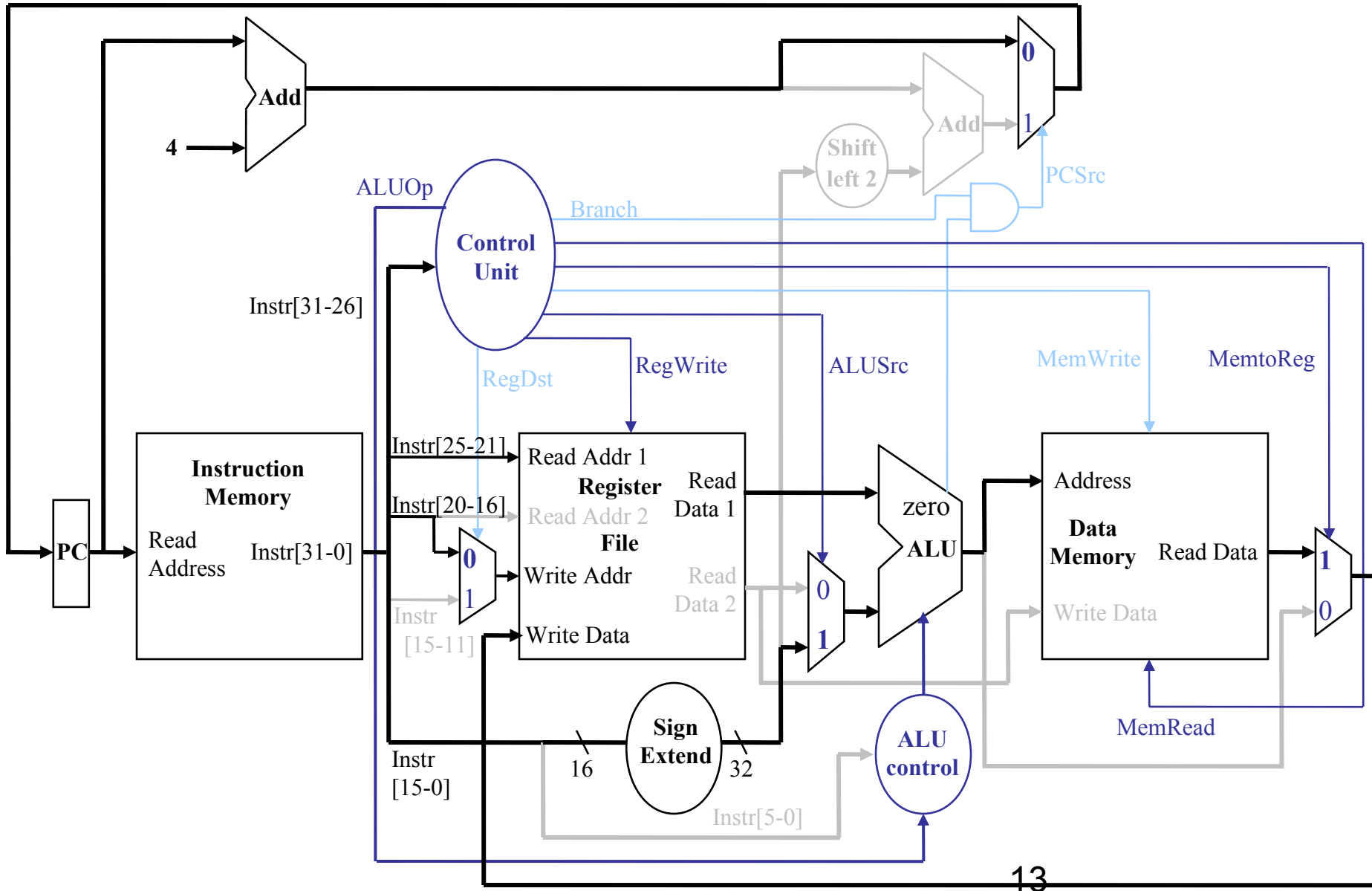


Branch on Equal Instruction

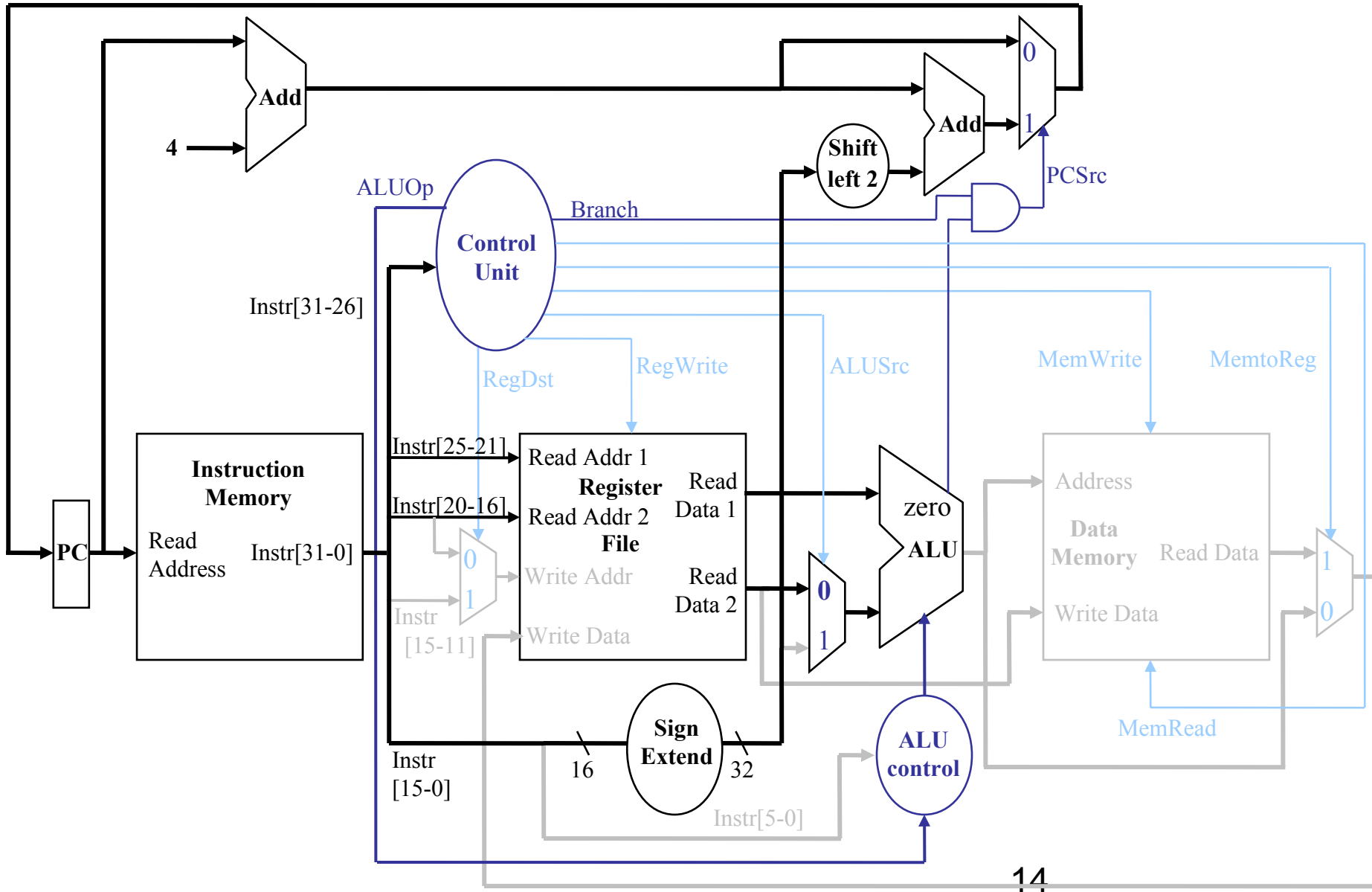


Adding the Jump Instruction

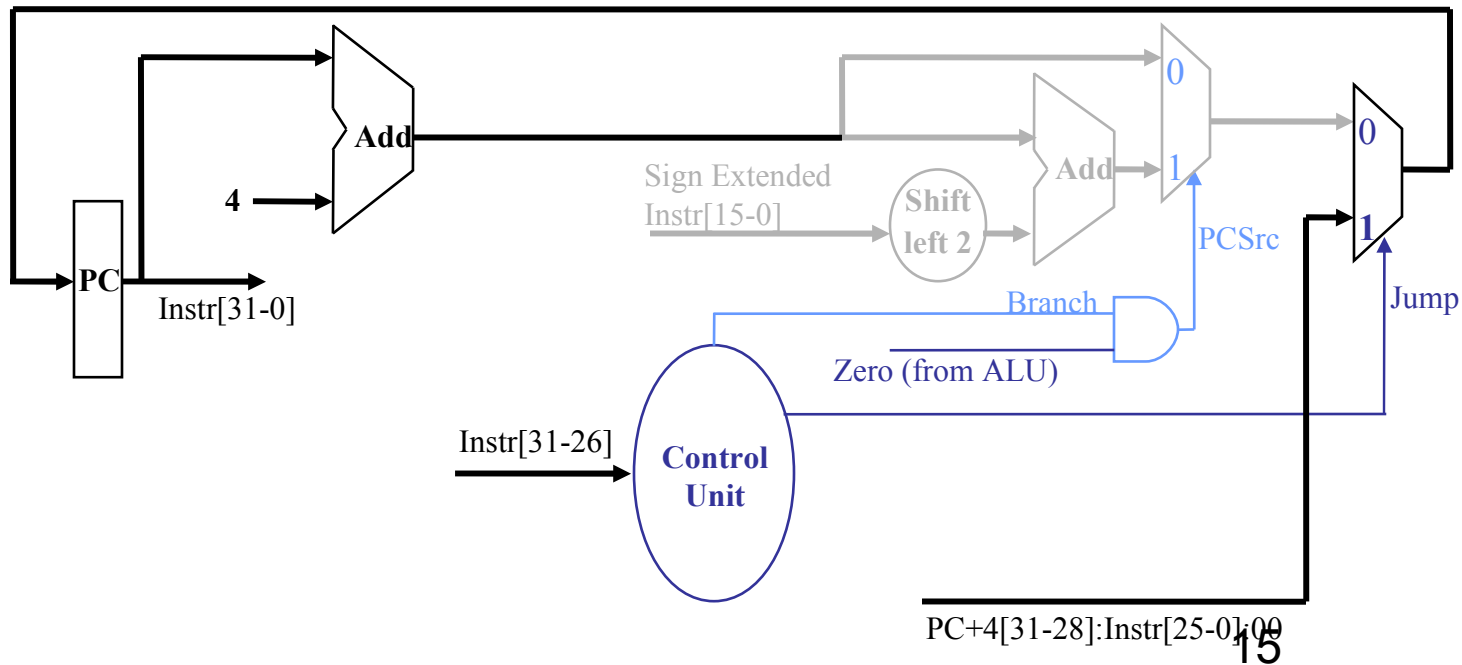- Additional multiplexer and control signal
- Jump address
 - 4 Most significant bits from PC + 4
 - 26 bits from instruction's address field
 - 2 zero bits



Single Cycle Characteristics

 - Uses the clock cycle inefficiently
 - The clock cycle must accommodate the **slowest** instruction
 - Especially problematic for more complex instructions (floating point multiply)



- Wasteful of area since some functional units (e.g., adders) must be duplicated because they can not be shared during a clock cycle
- But, it is simple and easy to understand