

Single Cycle Control

- Very simple
 - Control signals are functions of opcode and possibly function fields
 - Combinational logic suffices
- Ex: RegWrite
 - Asserted on `R-type`, `lw`
 - Deasserted on `beq`, `sw`, `j`


Multi-Cycle Control

- Much harder
 - Control signals depend on instruction and cycle
- Consider RegWrite

	Cycle				
Instruction	Fetch	Decode	Execute	Memory Access	Write Back
R-Type	0	0	0	1	
sw	0	0	0	0	
lw	0	0	0	0	1

- CPU must “remember” what cycle it is in
 - Control unit must maintain state
 - Several ways to do this


Review

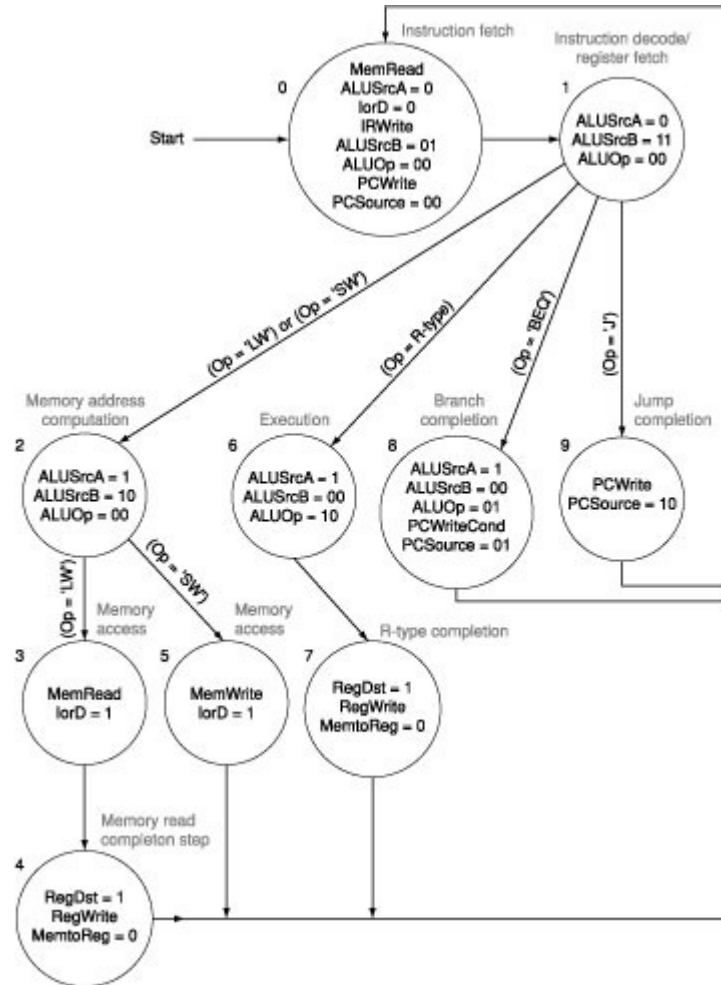

Multi-Cycle Control Implementation


- Two main control implementations
 - State machine
 - Translate finite state machine diagrams to hardware
 - Control signals function of current state
 - Microprogram
 - A small control program runs in parallel to CPU datapath
 - Program outputs are control signals
- Logically similar in many respects
 - Control “remembers” state and changes signals
 - Implementation very different
 - Combinations also possible

State Machine Control

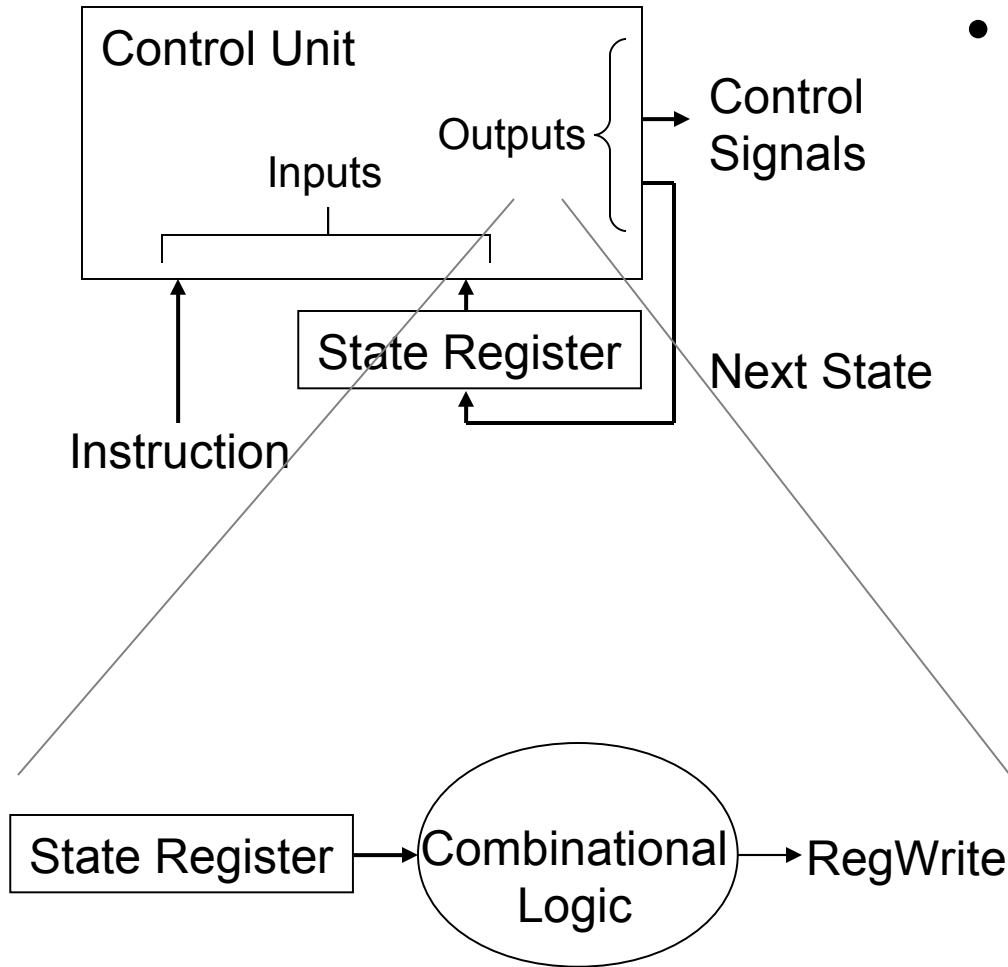


- From digital design:
 - Create state machine
 - Assign state values
 - Derive control signal functions
 - Derive next state functions

Microprogram Control

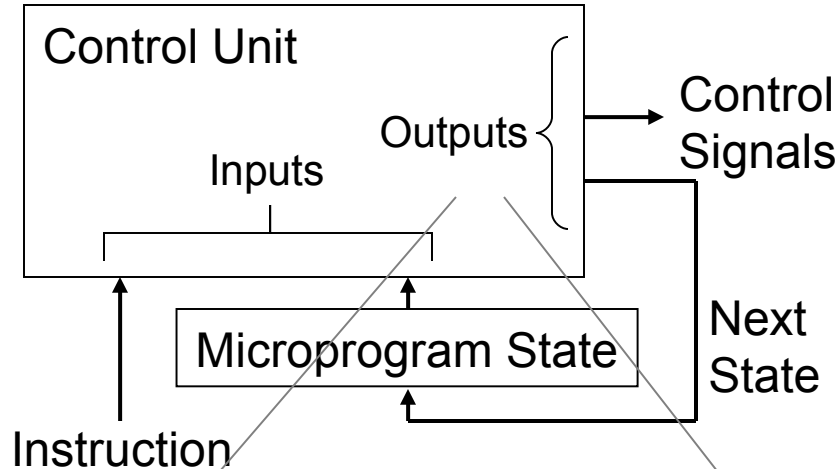

 - Control Unit is now an indexed ROM
 - Memory bits set control signals and next state
 - Microprogram state and instruction select the memory value




Single Microprogram ROM

- Inputs
 - 6 bits from instruction opcode
 - 4 bits from current state
- Outputs
 - 16 bits for control signals
 - 4 bits for next state
- ROM Size
 - 2^{10} 20-bit words
 - Total size: 20 kbits

Single Microprogram ROM

- ROM requires 20 kbits
- Many entries are redundant
 - Decode cycle always follows fetch cycle
 - Addresses XXXXXX 0000 always contain same value
 - $2^6 - 1 = 63$ wasted entries
 - Some inputs invalid
 - Addresses 111111 XXXX indicate invalid instruction
 - $2^4 - 1 = 15$ wasted entries per bad opcode
- Save space by dividing control into two ROMs
 - One ROM generates the next state
 - One ROM generates the control signals

Two Microprogram ROMs

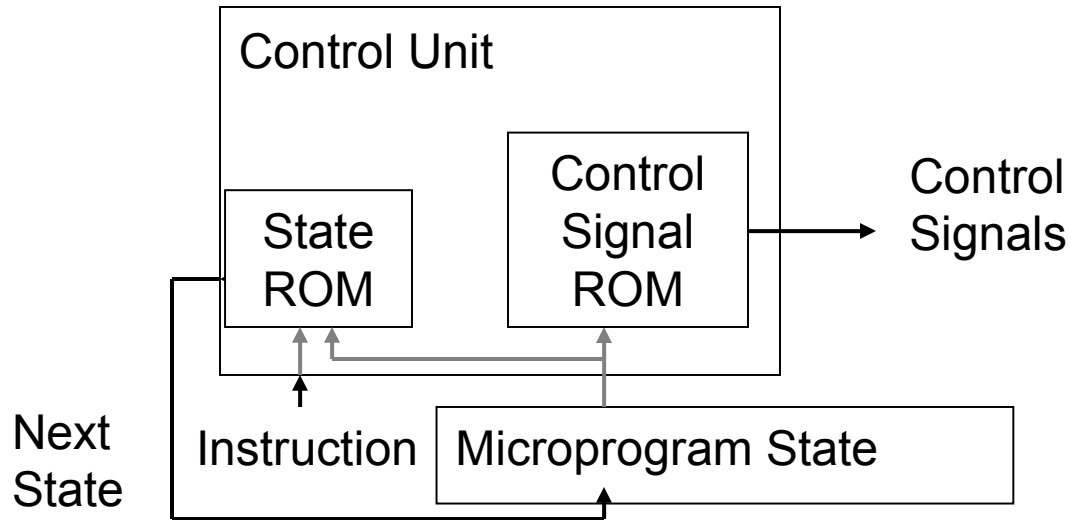


- Total ROM Size

- 2^{10} 4 bit words for State ROM
- 2^4 16 bit words for Control ROM
- $4096 + 256 = 4352 \approx 4.3$ kbits

Microprogram State ROM

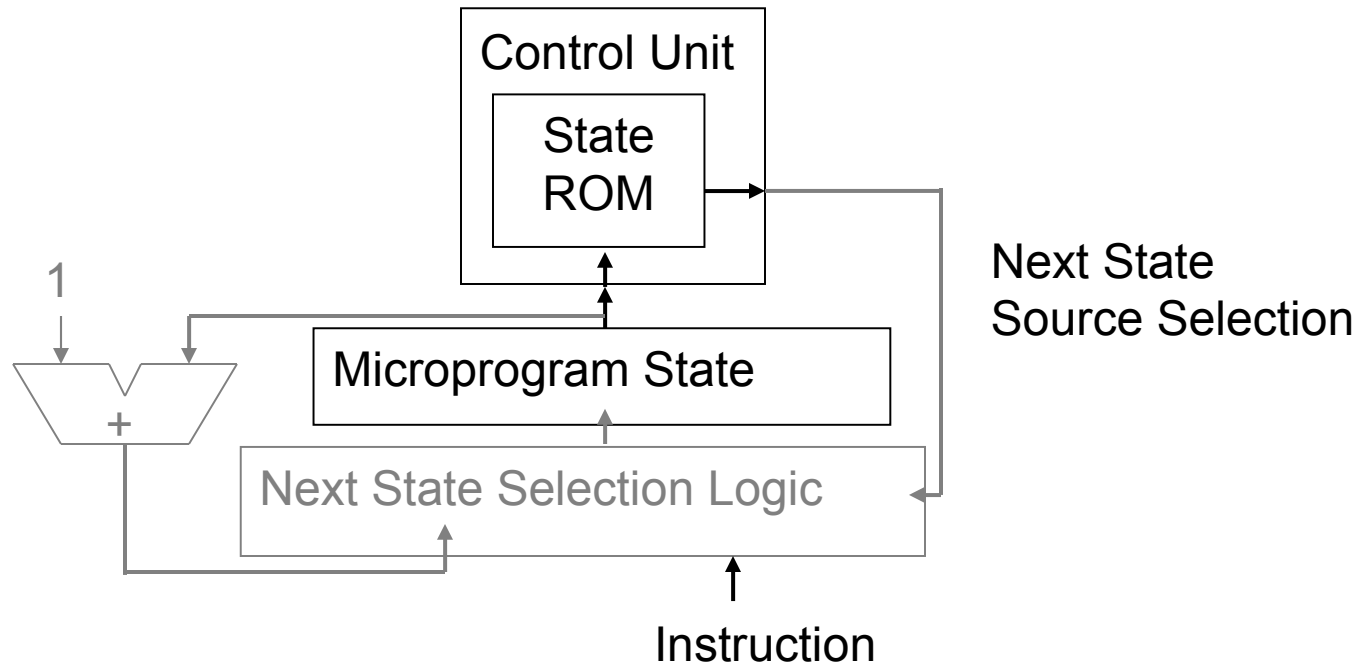- The State ROM still wastes space
 - Most states increment to next value
 - Select source of next state in microinstruction




-
-
- ROM Size 2^{10} 2 bit words = 2 kbits


Next State Selection Logic

- How to select next non-sequential state?
 - Combinational logic from opcode and current state
 - Use more ROMs!
- Use dispatch ROM to “jump” in microprogram
 - opcode used as input to dispatch table
 - Next state produced as output
 - Use one dispatch table per decision point

Dispatch ROM Points

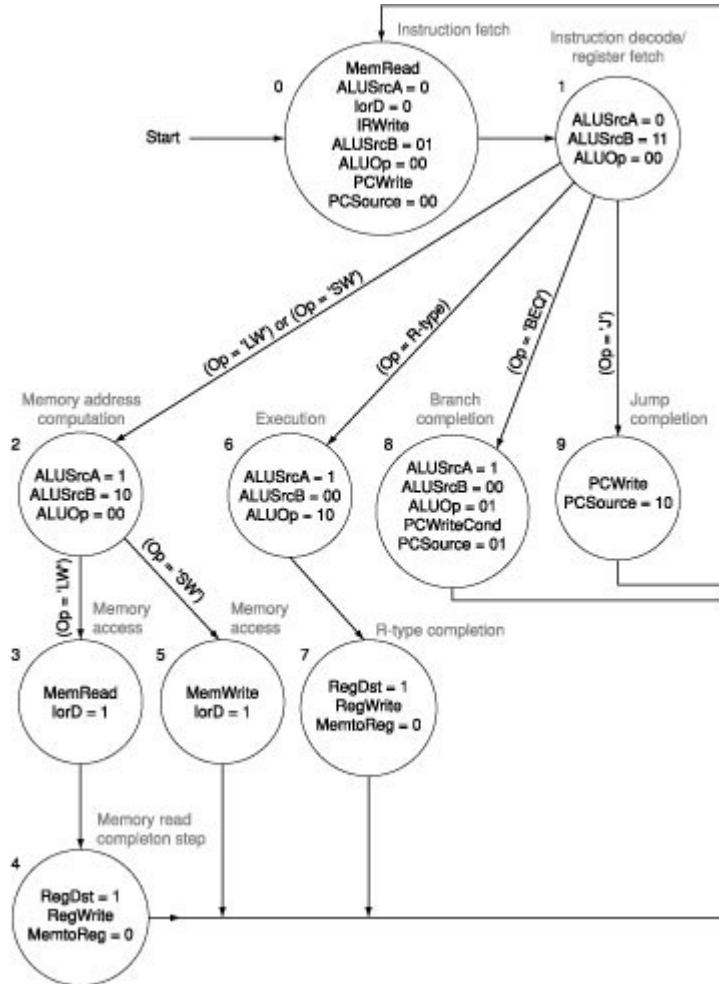


Dispatch ROM Points

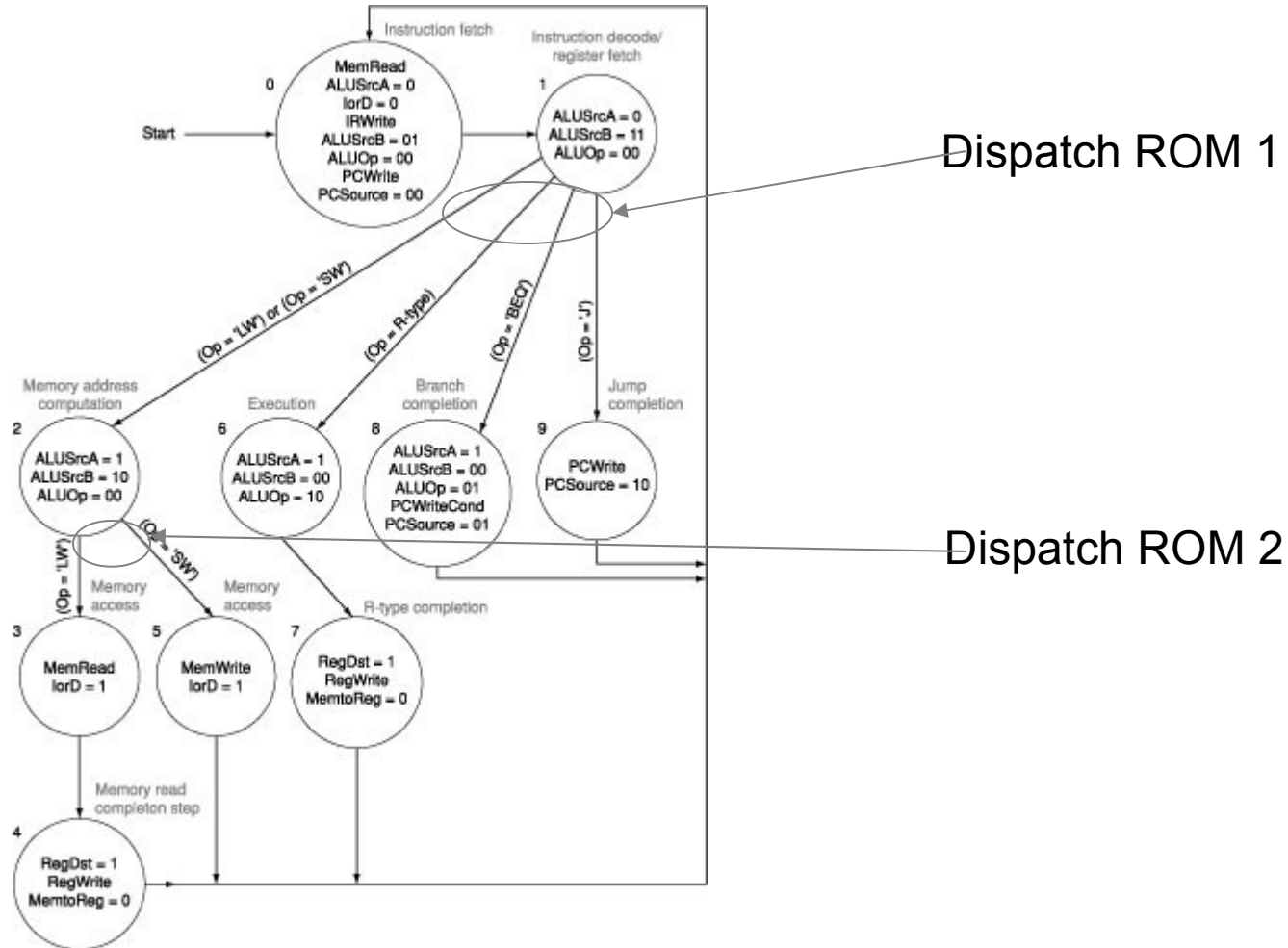

Microprogram ROM Size

- Control signal ROM
 - 2^4 16 bit words
 - 256 bits
 - Next state ROM
 - 2^4 2 bit words
 - 32 bits
 - Dispatch ROMs
 - 2 ROMs at 2^6 4 bit words
 - 512 bits
 - Total ROM size = 800 bits
 - Still many other ways to reduce size
- Same inputs, so combine into a single ROM.

Final Microprogram Control Design

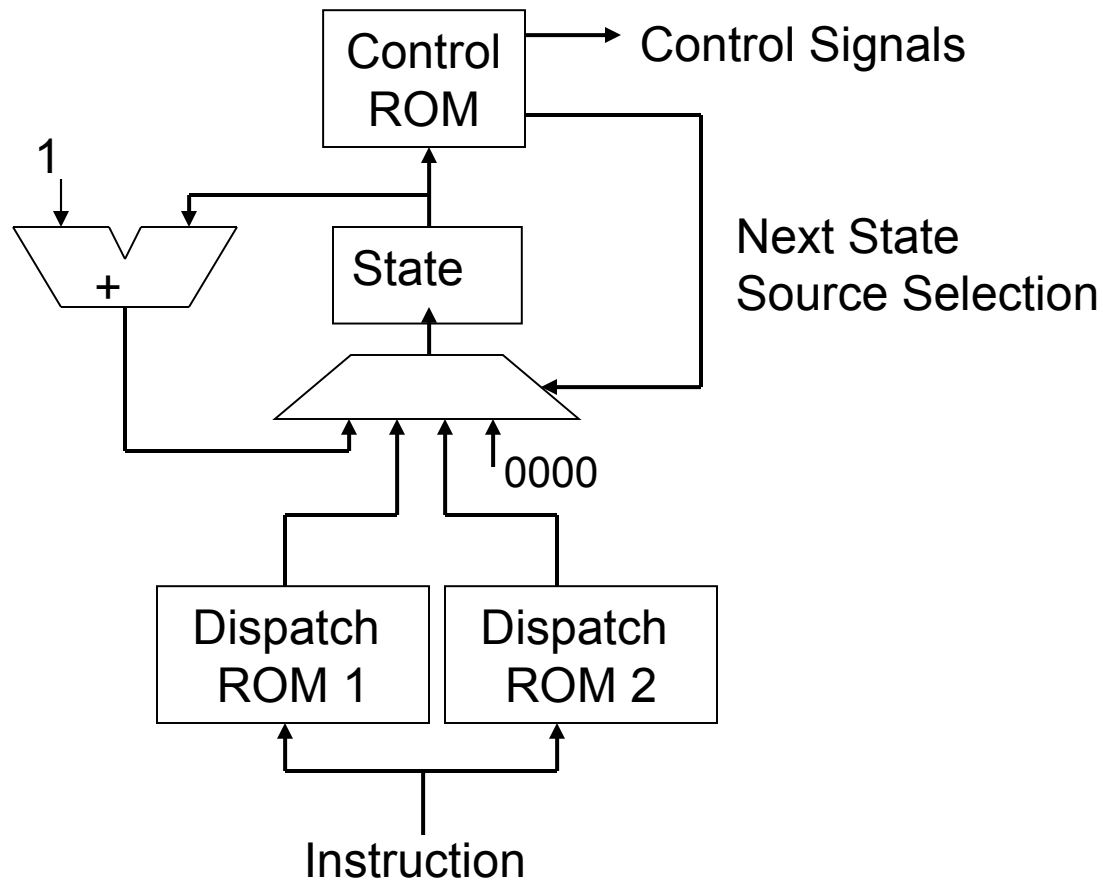

Control ROM Format

- Each entry 18 bits wide
 - 16 leftmost bits drive control signals
 - Order signals according to Figure C.3.6
 - PCWrite = M[17]
 - ...
 - RegDst = M[2]
 - 2 rightmost bits select next state source (M[1:0])
 - 00: Next state = 0000
 - 01: Use dispatch ROM 1
 - 10: Use dispatch ROM 2
 - 11: Increment state

Microcode Generation

- Creating the memory entries manually is difficult and error prone for real designs
 - Analogous to programming in machine code
- Microassemblers can perform that function
- What “language” to use?
 - Microinstructions
 - Similar to assembly language
 - See section 5.7
 - Register Transfer Language
 - Describe operations at the hardware level
 - For example, $A \leftarrow \text{Reg}[\text{IR}[25:21]]$

Fetch: Control Signals in Microcode

- All the signals
- Some are don't care
 - MemtoReg
 - RegDst
- Some, not listed in FSM diagram, need a value
 - MemWrite
 - RegWrite

Signal	Value
PCWrite	1
PCWriteCond	0 or X?
lorD	0
MemRead	1
MemWrite	0
IRWrite	1
MemtoReg	X
PCSource1	0
PCSource0	0
ALUOp1	0
ALUOp0	0
ALUSrcB1	0
ALUSrcB0	1
ALUSrcA	0
RegWrite	0
RegDst	X

Fetch: Next State Selection

- Decode always comes after Fetch
 - Next state control = 11 (increment)
 - Assumes Decode State = Fetch State + 1

Fetch Cycle Microcode Entry

- Assume Fetch cycle assigned 0000
- Now, combine control signal portion with next state selection
- Control ROM entry for address 0000

• MIF Entry

1001010000001000 11

0x0 : 0x25023;

Encoding Control Signals

- Consider the IRWrite signal

	0000	0001	0010	0011	0100	0101	0110	0111	1000
IRWrite	1	0	0	0	0	0	0	0	0

- Only asserted during Fetch cycle
- Can we save space by combining signals to generate IRWrite or remove IRWrite?
 - No signal duplicates IRWrite, so no replacement
 - Consider the PCWrite and MemRead signals

	0000	0001	0010	0011	0100	0101	0110	0111	1000
PCWrite	1	0	0	0	0	0	0	0	1
MemRead	1	0	0	1	0	0	0	0	0

- See any pattern?