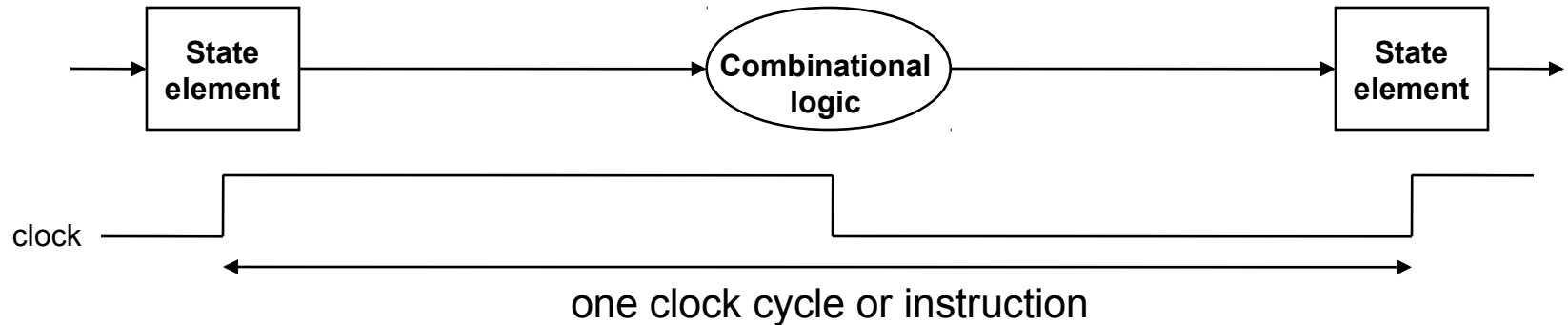



# Multi-cycle Approach

- Single cycle CPU




- Multi-cycle CPU

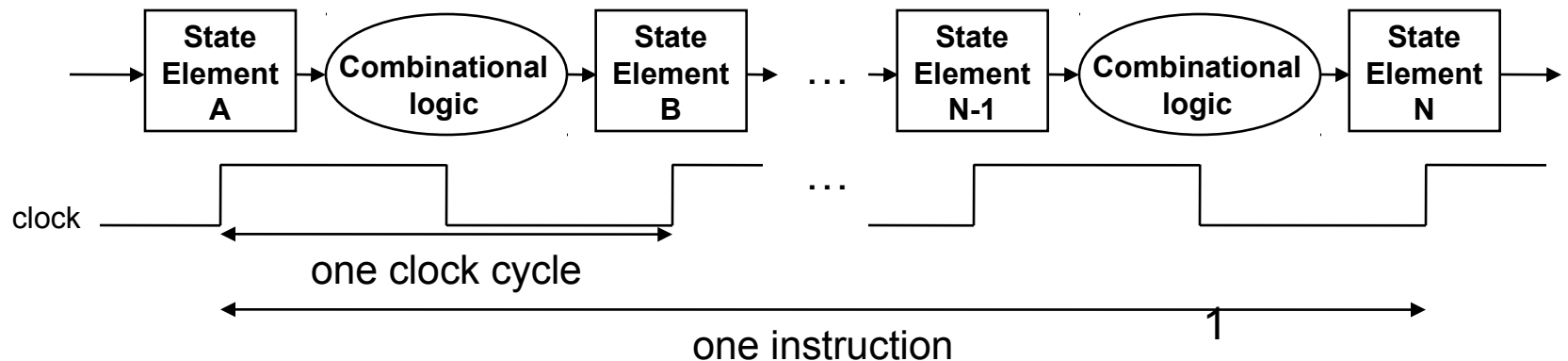– Requires state elements to hold intermediate values


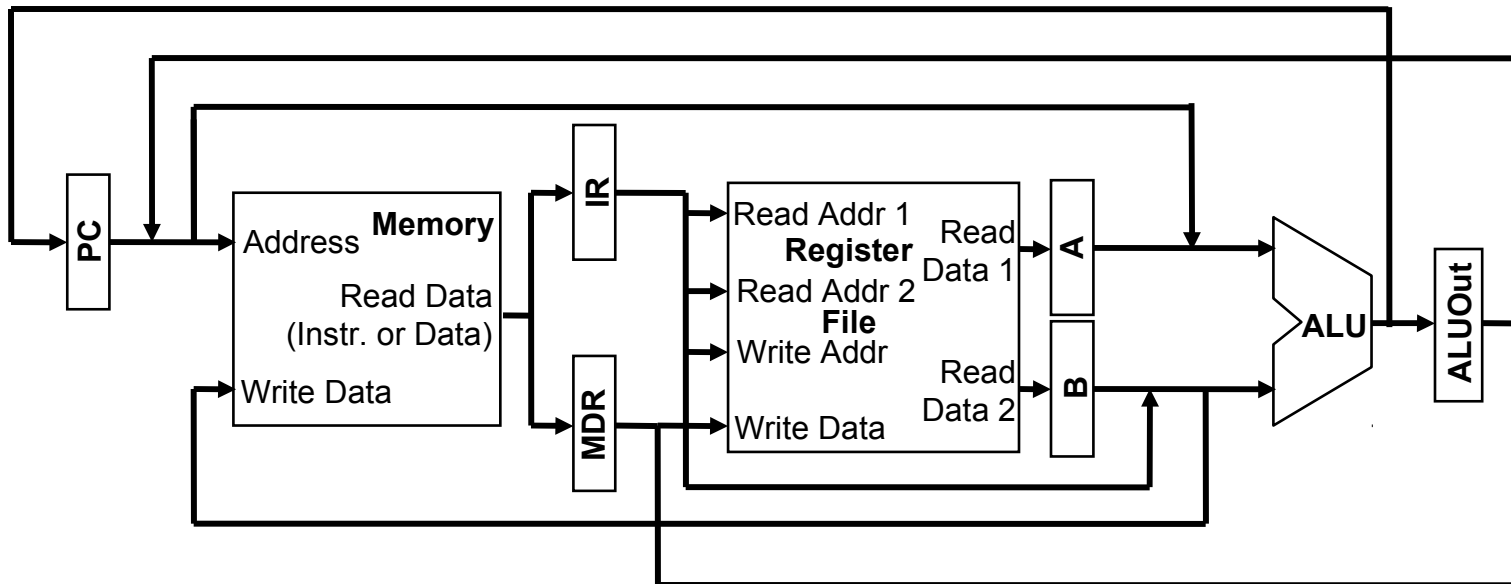
# Multi-cycle Approach

- Each cycle must
  - Store values needed in a later cycle of the current instruction in an internal register. All except IR hold data for one clock cycle.



**IR** – Instruction Register      **MDR** – Memory Data Register

**A, B** – Register File data      **ALUOut** – ALU Result Register


- Store values needed by subsequent instructions in the register file or memory

# Multi-cycle Control

---

- New control signals needed
  - **PCWriteCond** is set during a beq instruction
    - Formerly called Branch signal
  - **PCWrite** is set to write PC
    - Unconditional write signal needed during Fetch cycle
  - **lorD** controls what address is used for the memory
    - PC holds address for fetch cycle
    - ALUOut holds address for memory access instructions
  - **IRWrite** controls when the IR is written
  - **ALUSrcA** control one input to ALU
    - rs register for most operations
    - PC for branch instructions
    - Old ALUSrc renamed ALUSrcB and expanded

# Multi-cycle Control and Datapath

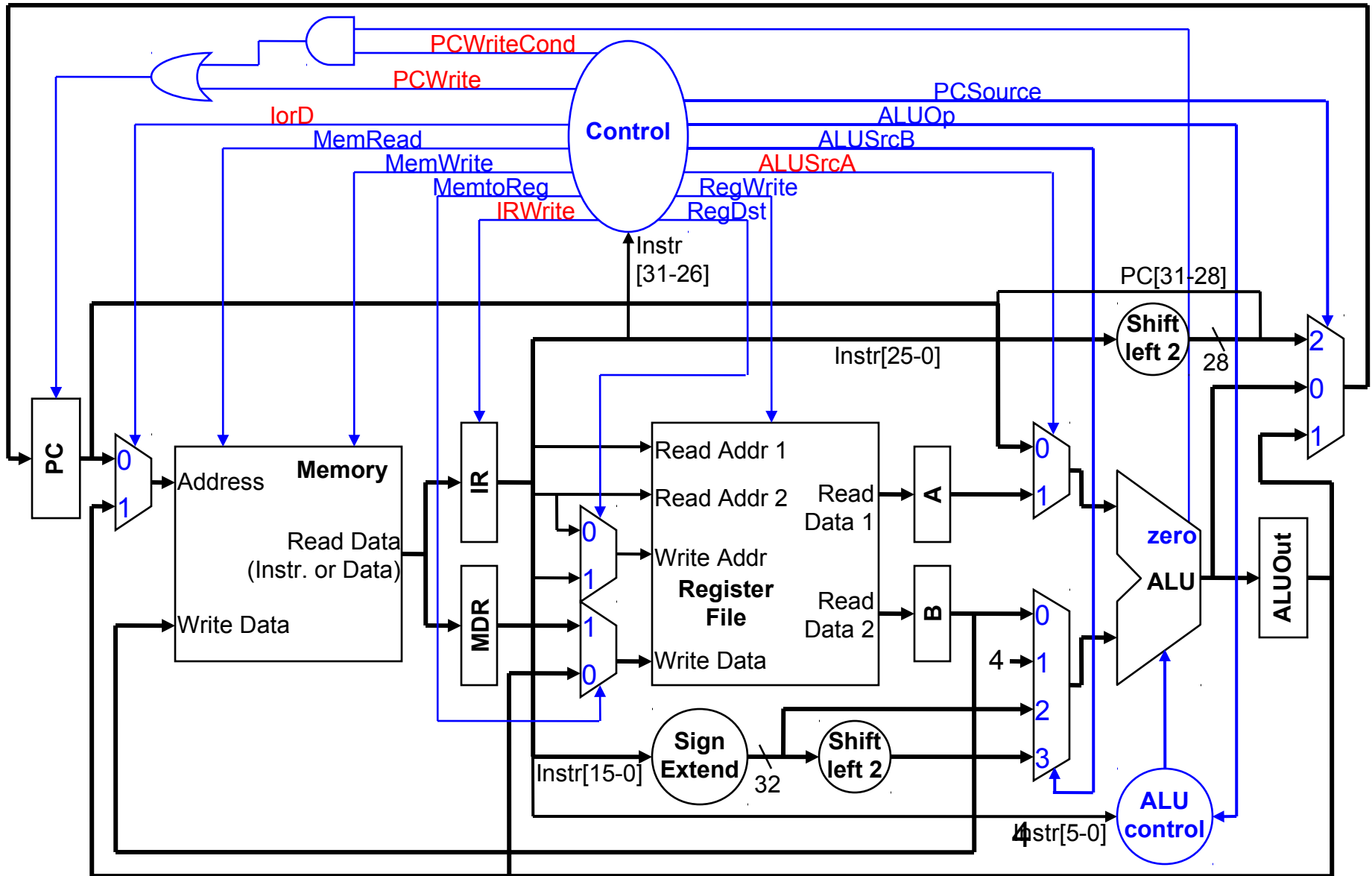

# Multi-cycle Steps

---


- Instruction Fetch
- Decode and Register Fetch
- Execution
- Memory Access
- Write Register File

# (1) Instruction Fetch Cycle

---

- Increment PC using ALU
  - $PC = PC + 4$
- Read instruction from memory
  - $IR = M[PC]$
- Control signals must
  - Select memory address source
  - Enable memory reading
  - Enable PC and IR write
  - Select PC source
  - Select ALU input as PC and constant 4
  - Select ALU operation (addition)

# Instruction Fetch

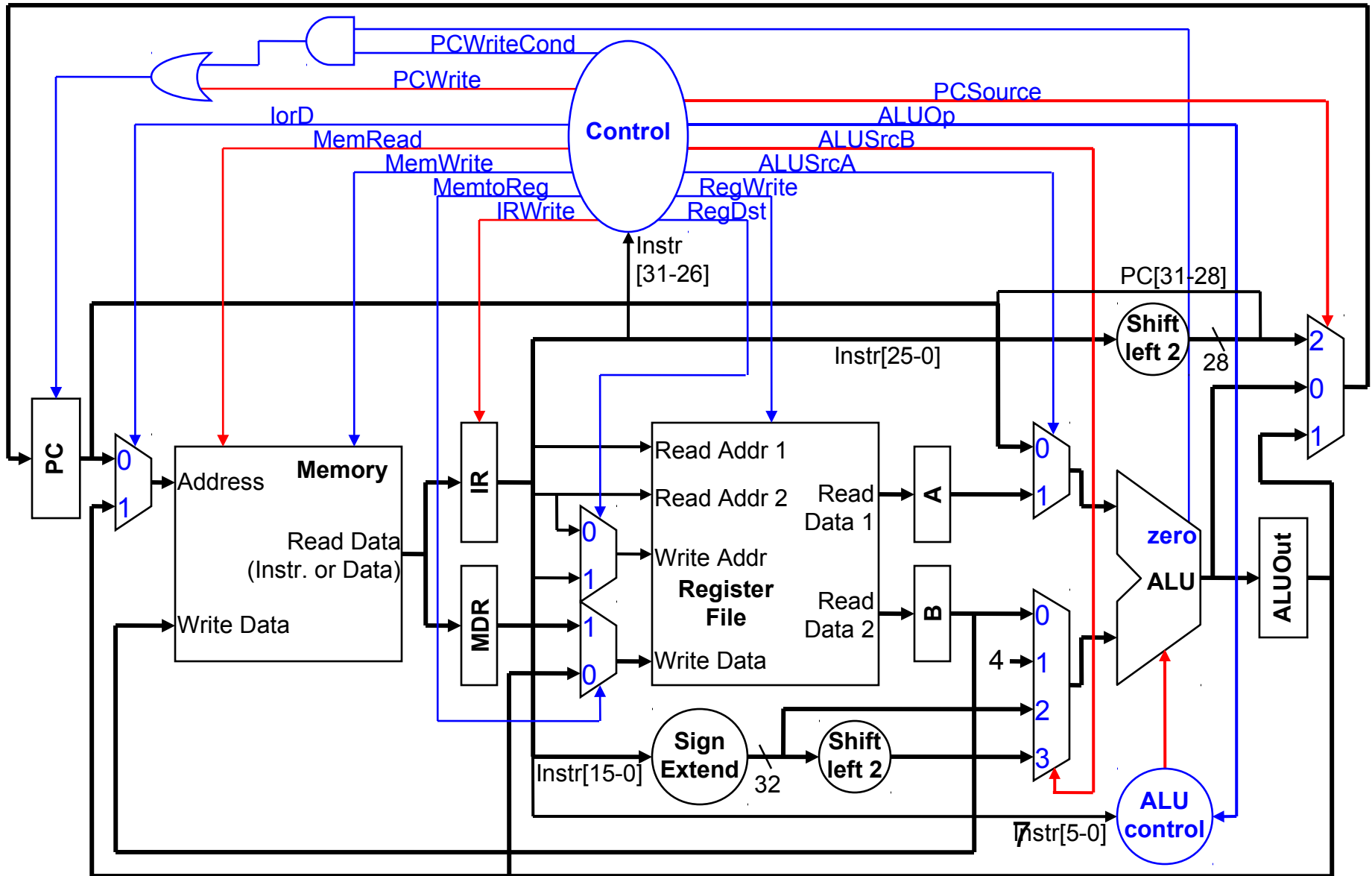


## (2) Decode and Register Fetch Cycle

---

- Read register values
  - $A = R[rs]$ ,  $B = R[rt]$
- Compute branch destination
  - $ALUOut = PC + \text{sign extended immediate value}$
- Prepare for next step based on instruction
- Control signals must
  - Select ALU inputs as PC and immediate value
  - Select ALU operation (addition)



# Decode and Register Fetch

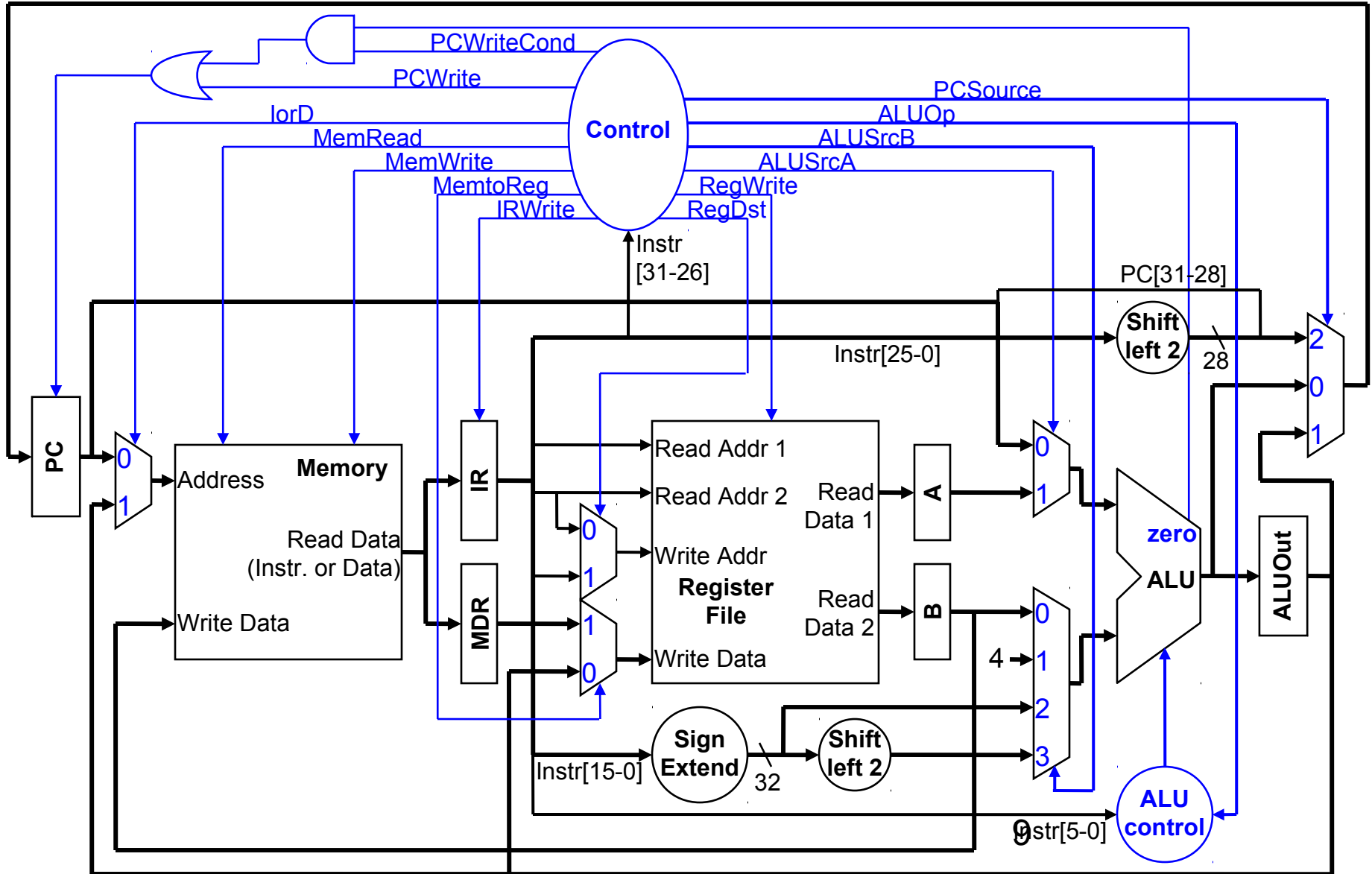


# (3) Execution Cycle

---

- Functionality varies with instructions
  - Memory reference
    - Compute address
    - $ALUOut = A + \text{sign extended immediate}$
  - R-type
    - Compute operation
    - $ALUOut = A \text{ op } B$
  - Branch
    - Store new PC if needed
    - $PC = ALUOut$
    - ALUOut contains branch destination from previous cycle
- Control signals will depend on instruction type
  - Mem/R-type: Select ALU input and operation
  - Branch: Select PC source and set PC write control signal if needed

# Execute Branch

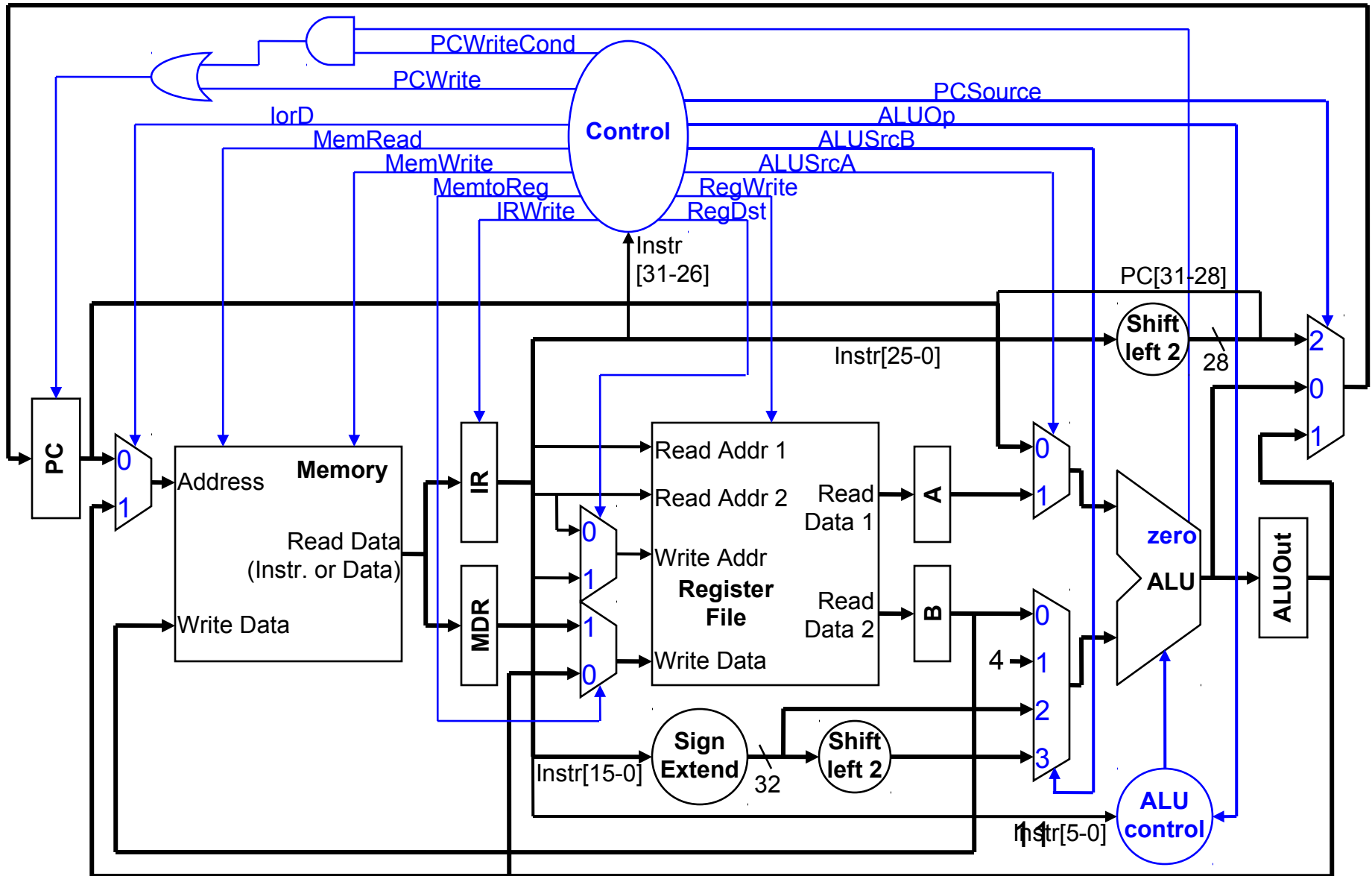


# (4) Memory Access Cycle

---

- Functionality varies with instructions
  - Memory reference
    - Read memory (lw) or write memory (sw)
    - $MDR = M[ALUOut]$  or  $M[ALUOut] = B$
  - R-type
    - Write result to register file
    - $R[rd] = ALUOut$
- Control signals will depend on instruction type
  - Memory reference
    - Enable memory read or write
    - Select memory address
  - R-type
    - Select register file write address and data
    - Enable register file write

# R-Type "Memory Access"

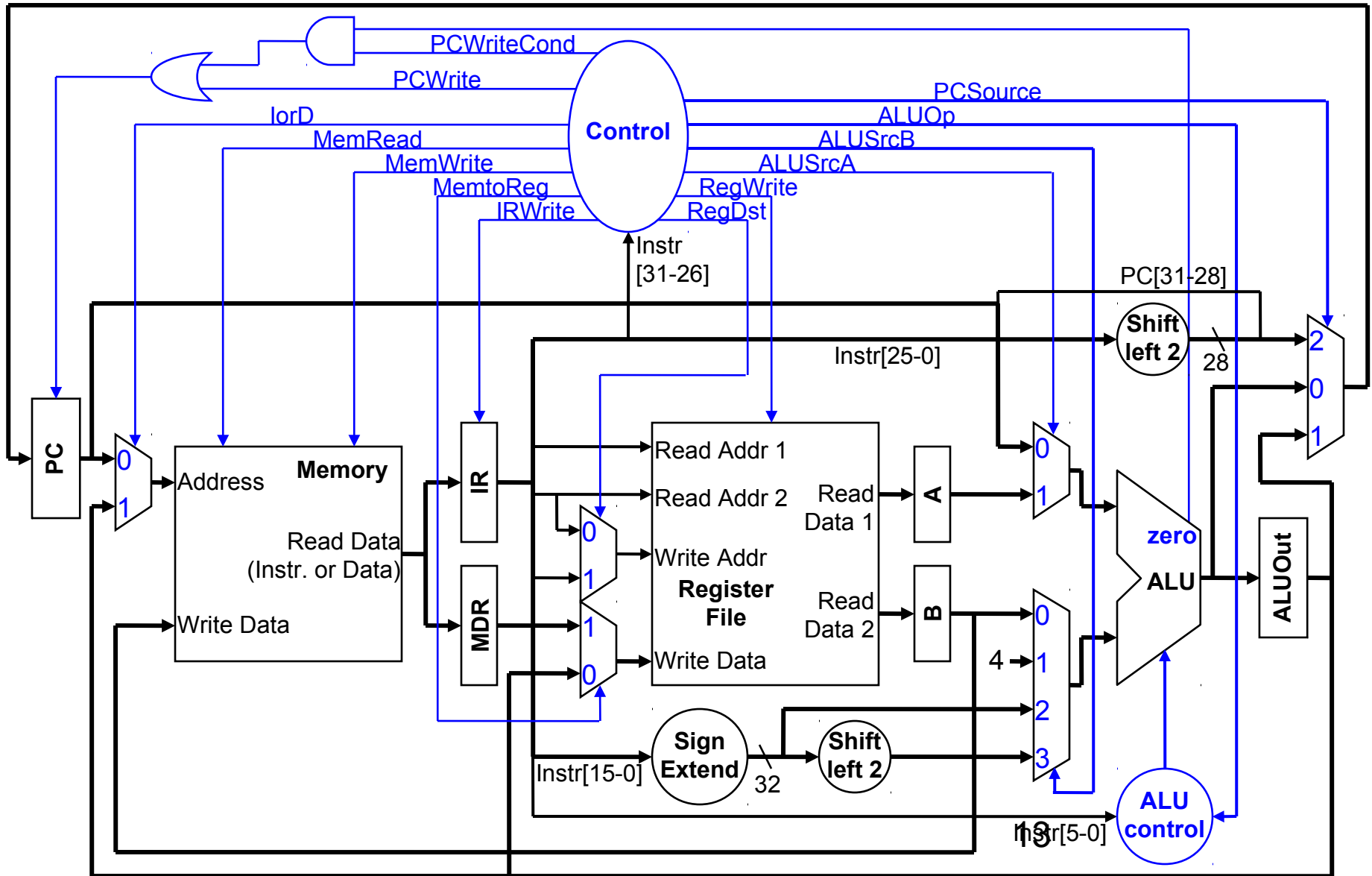


## (5) Write Register File Cycle


---

- Only used by load instructions
- Write memory value to register
  - $\text{Reg}[\text{rt}] = \text{MDR}$
- Control signals must
  - Enable register file write
  - Select register file write address and data

# Iw Write Registers

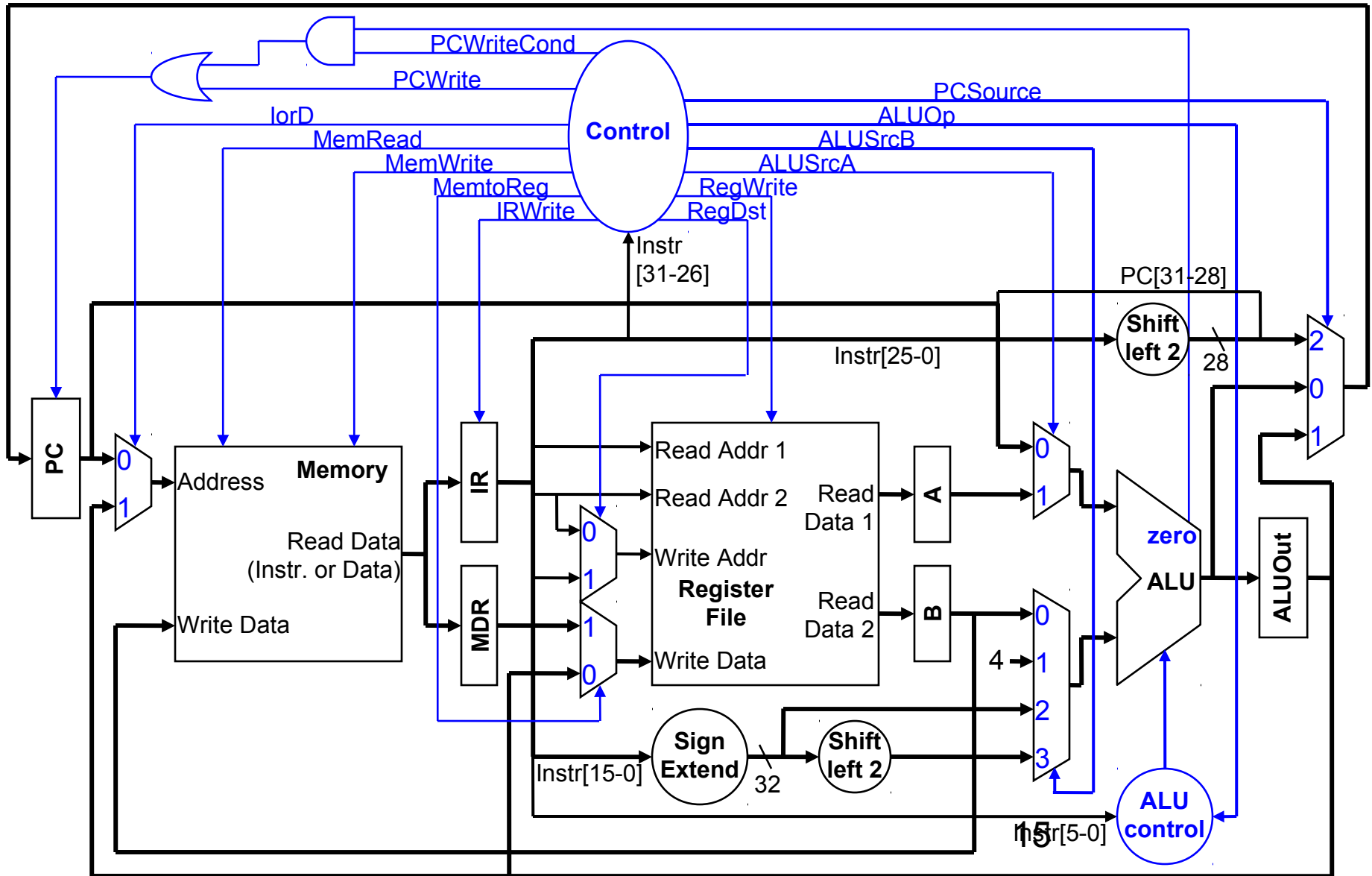

# Review

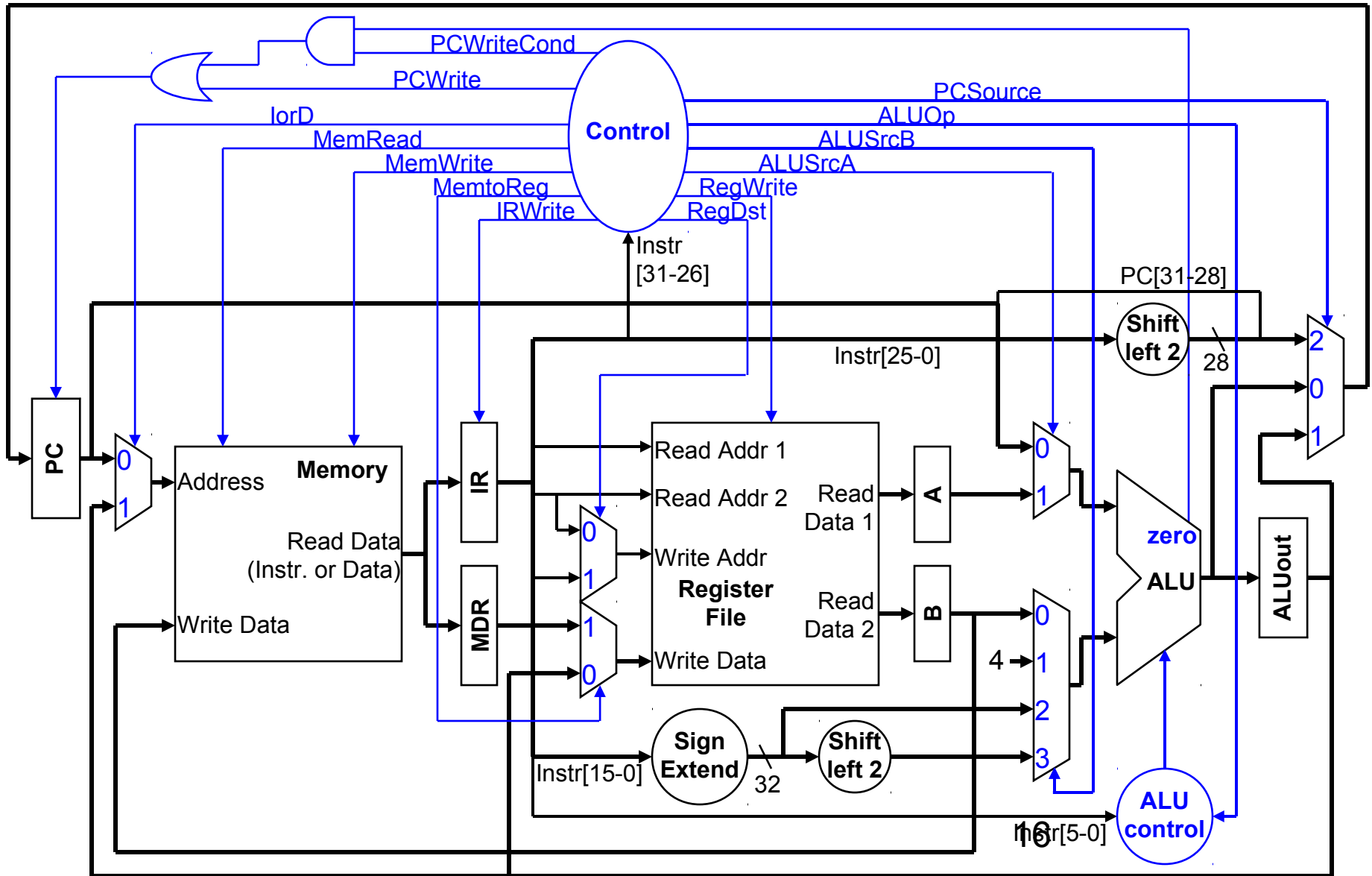




# Defining the CPU Control

---


- Use a finite state machine model to design the control
  - Control now has state or memory
  - Action depends on input and current cycle
- Signal names in each state are asserted
  - Asserted signals are set or enabled
  - Unlisted signals are deasserted
- Arcs between states list conditions for transition
 
## • Example State A


- Signal Run is asserted
- Goes to State B when input Up = 0
- Goes to State C when input Up = 1




# Instruction Fetch and Decode Cycles

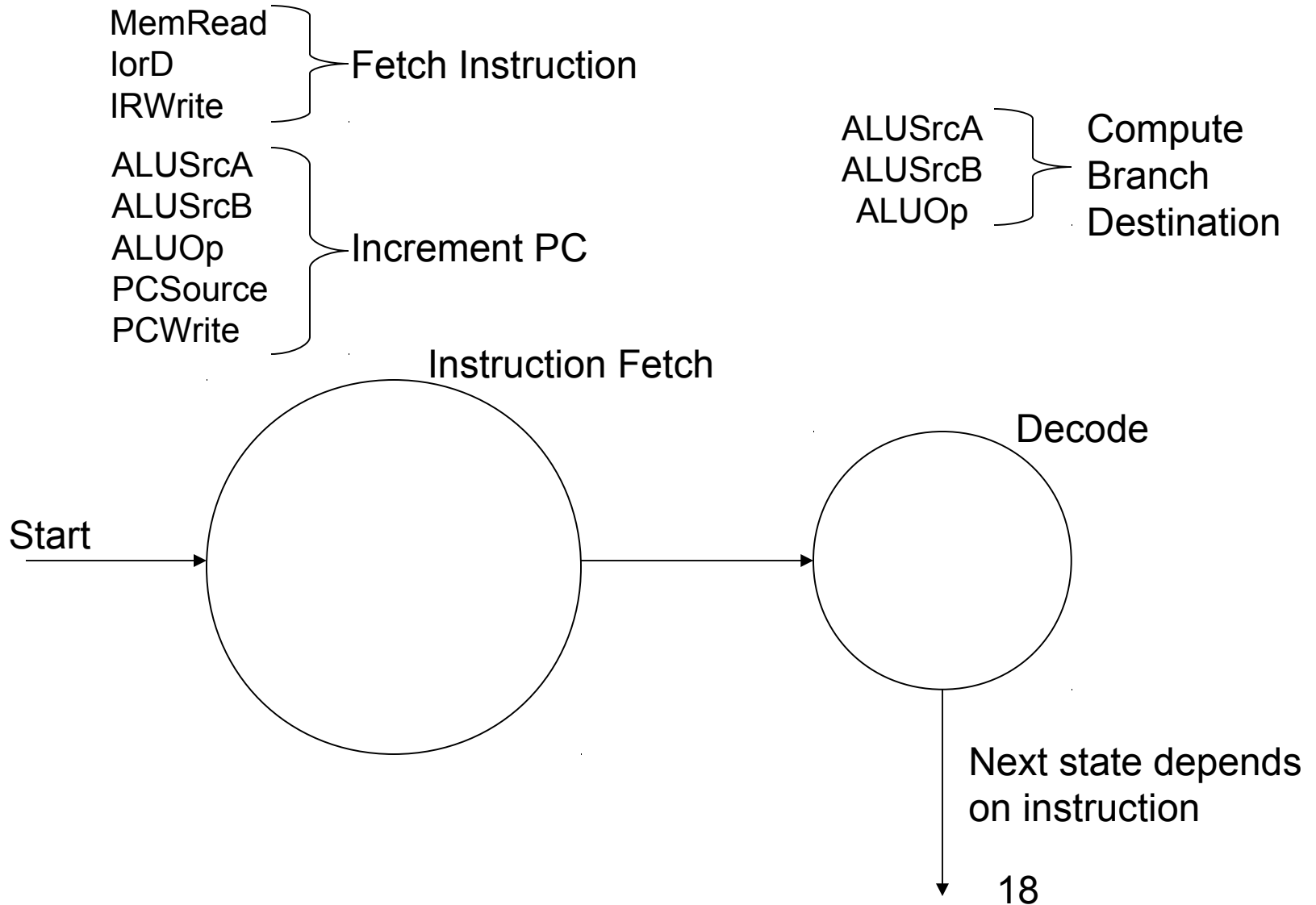

# Instruction Fetch and Decode Cycles

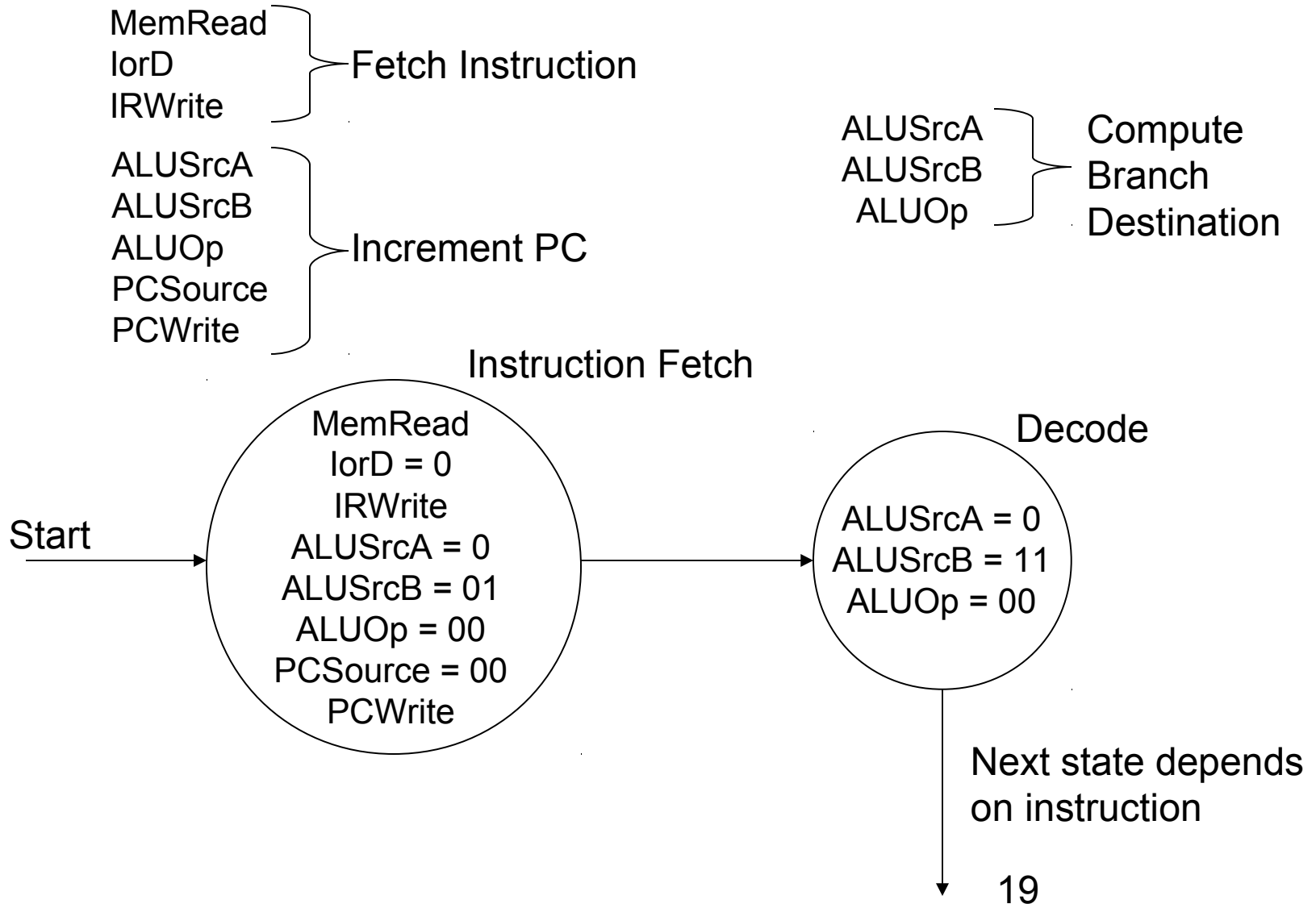


# Memory Access Instructions

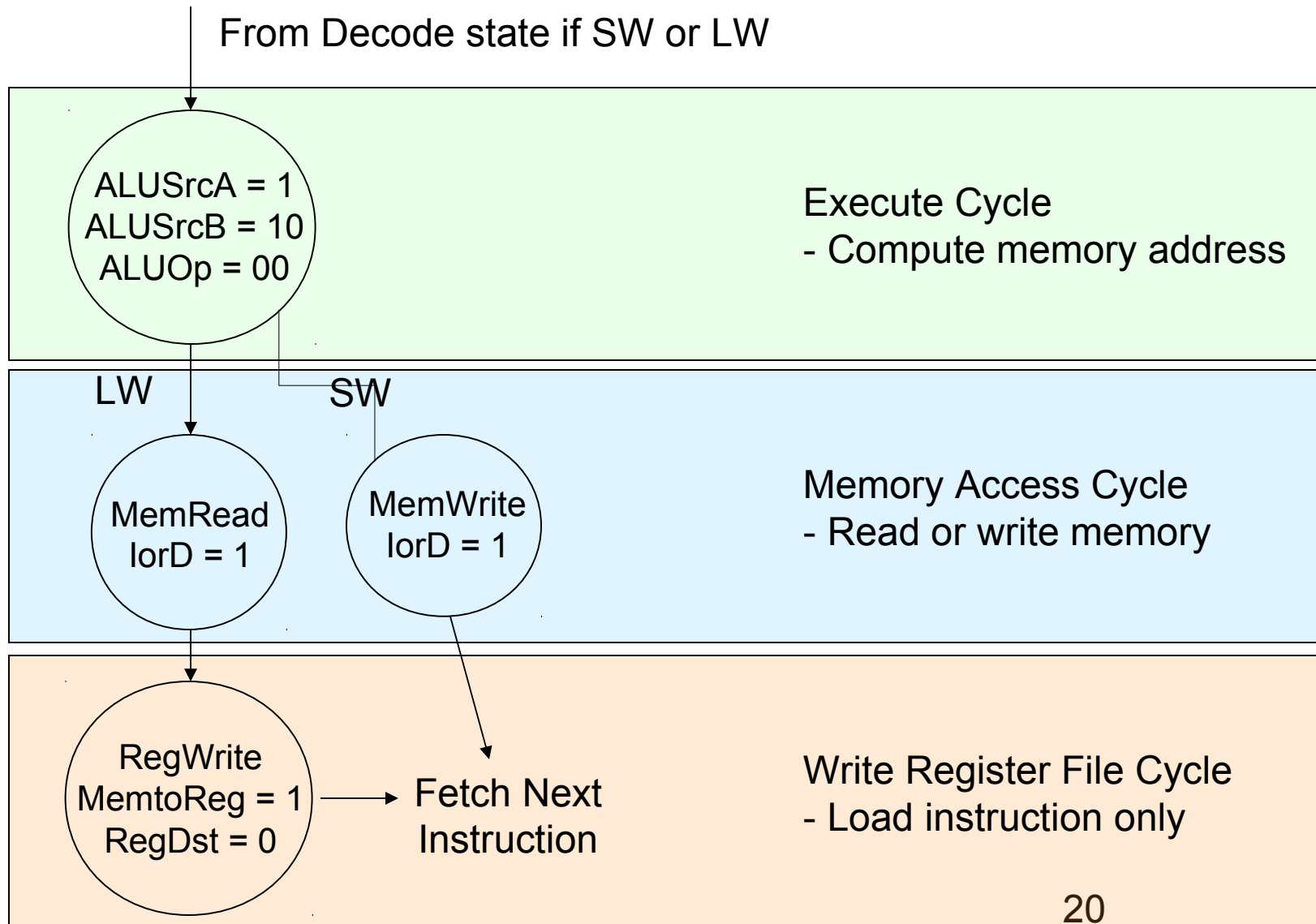

# R-type Instructions

---

From Decode state if R-type

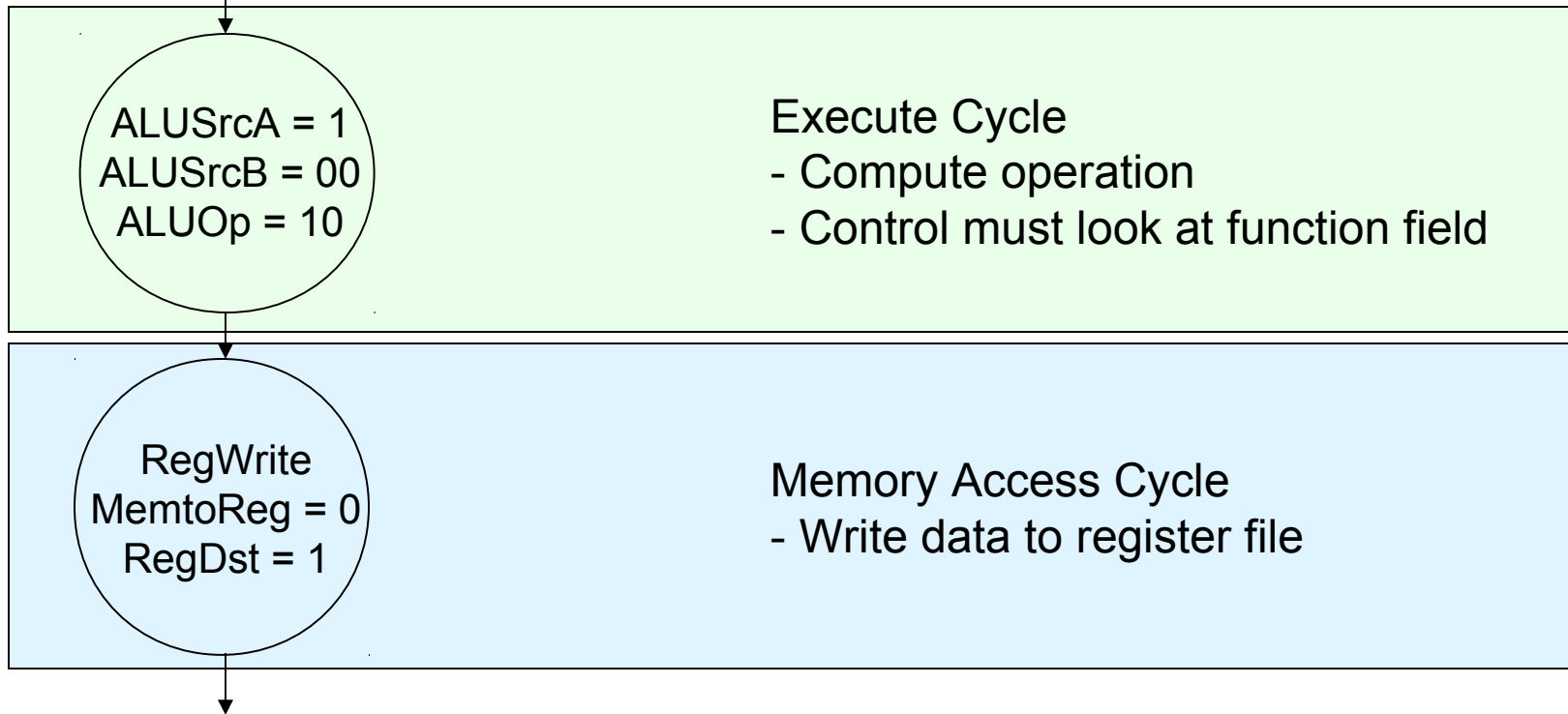


Fetch Next  
Instruction

# Branch on Equal Instruction


---

From Decode state if BEQ

 

Fetch Next  
Instruction

# Final State Diagram

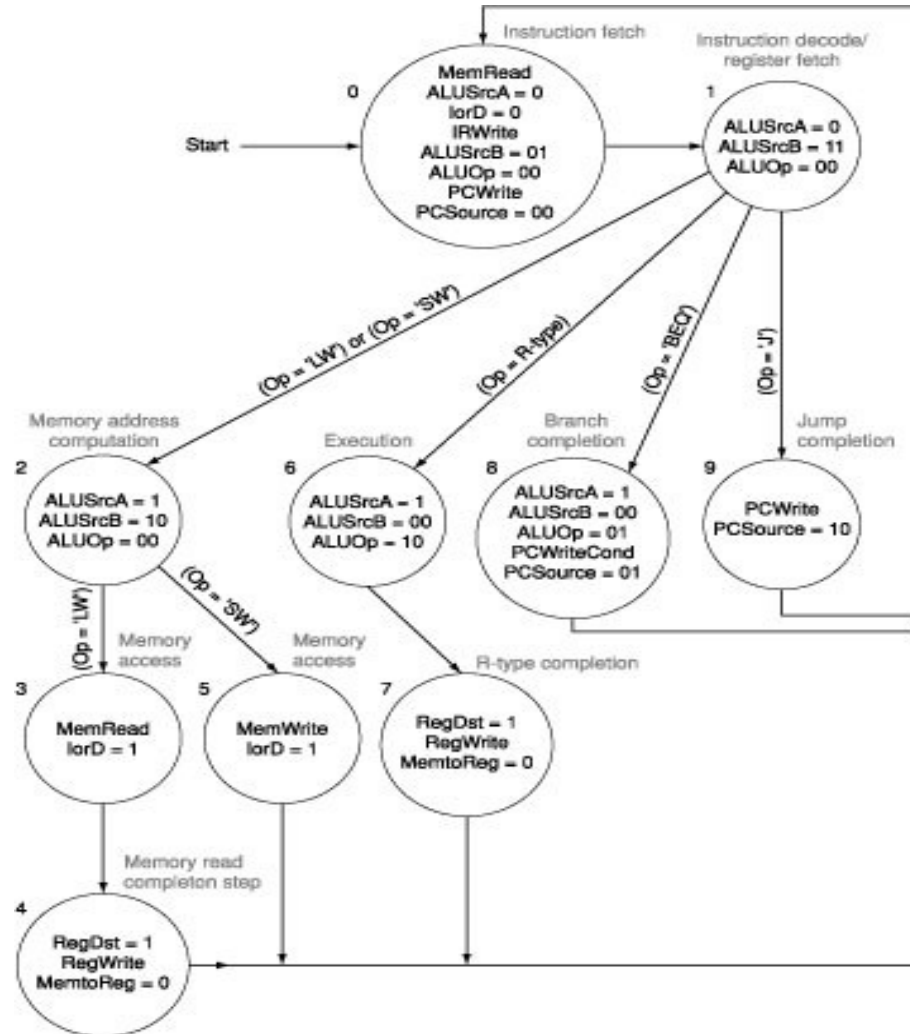

# Implementing jal

---

- Jump and link (jal)


- J-Type
- PC+4 → \$31
- Jump destination → PC

- What modifications are required?

- 2 Cycle
  - Const 31 write destination
  - Expand PCSource mux with ALUOut as PC+4
- 3 Cycle
  - Const 31 write destination
  - PC connected to write data



# Implementing jal

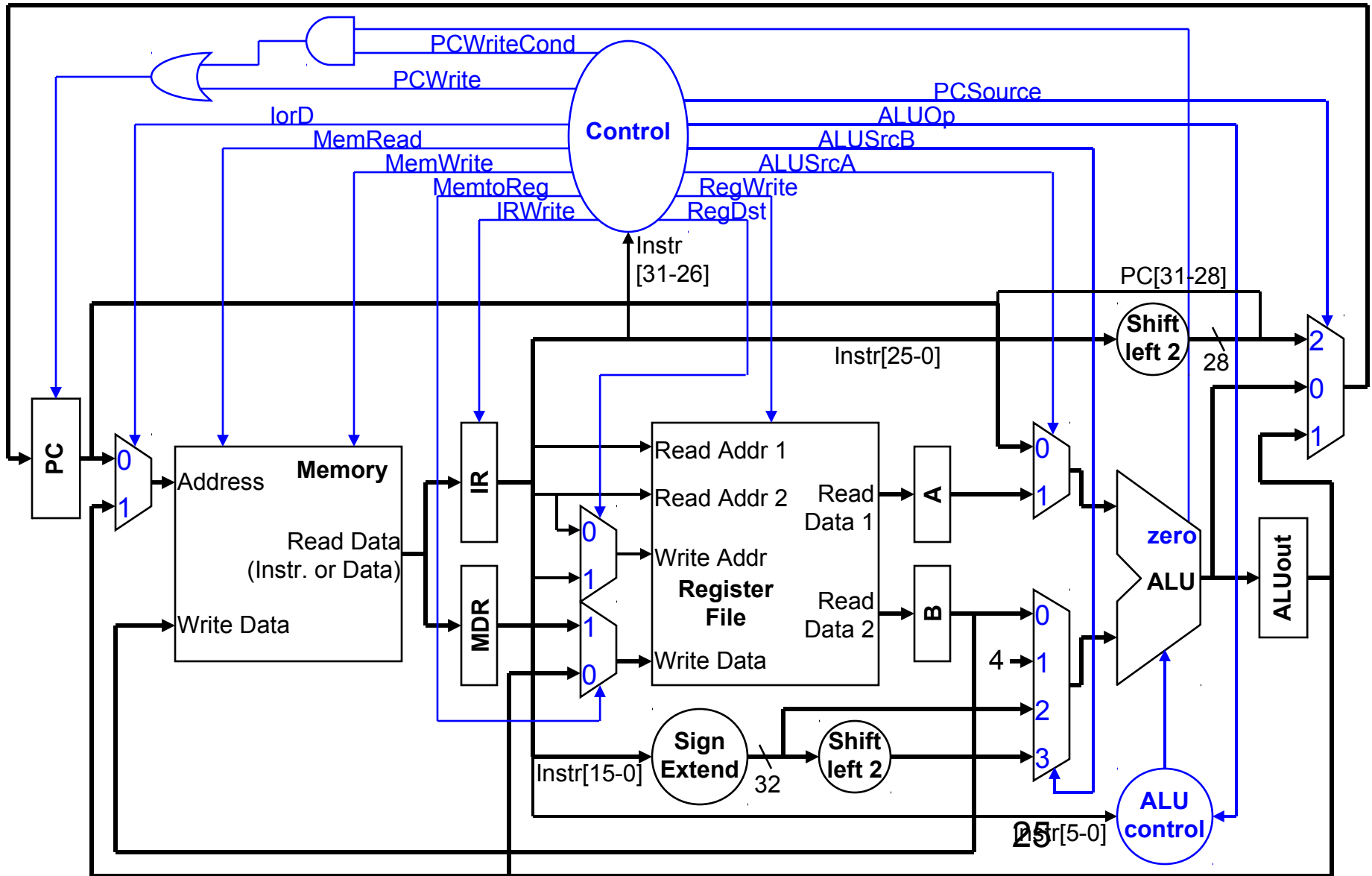

# Implementing jal (needs fixing MF)

