1. (10 pts) **We're going to play Final (exam) Jeopardy!** Associate the following answers with the appropriate question. (You are given the "answers": Pick the "question" that goes best with each "answer".) The first one has been done for you.

"Answers:"

- z. Anywhere but here. **v**
- 1a. A Flip Flop.
- 1b. A binary digit appended to a group of binary digits to make the sum of all the digits either always odd or always even.
- 1c. A structure that holds recent mappings of virtual to physical addresses.
- 1d. To make Memory appear to cost as much as the cheapest element and perform as well as the fastest element.
- 1e. Memory that goes away when the power is turned off.
- 1f. What happens when a page is referenced but not in memory.
- 1g. A technique in which an I/O device is periodically checked to see if it needs service.
- 1h. A technique used in CD-ROM Drives to increase storage density.
- 1i. To maximize the efficient use of an expensive system.
- 1j. A type of memory that uses capacitors to store data.

"Questions:"

- a) What is synchronous timing?
- b) What is asynchronous timing?
- c) What is a circuit that exhibits purely sequential behavior?
- d) What is the Data Bus?
- e) What is a Parity bit?
- f) What is a Register?
- g) What is a Cache?
- h) What is DMA?
- i) What is an Address Translation Lookaside Buffer (or TLB)?
- j) What is an interrupt?
- k) What is the goal of the Memory Heirarchy?
- l) What is a Page?
- m) What's the point to using a Base Page Table?
- n) What is Volatile memory?
- o) What is a Page Fault?
- p) What is Non-Volatile memory?
- q) What is polling?
- r) What is Constant Linear Velocity?
- s) What is Constant Angular Velocity?
- t) What is the goal of multiprogramming?
- u) What is Dynamic RAM?
- v) Where would I rather be right now than where I am?

2. (3) In the Cache you designed in Lab 4, what 3 signals are checked to decide which specific cache block to write to?

3. (4) In the Cache lab, you used and MRU circuit to decide which line should be replaced. Show that circuit, and also show how it could be modified to make it track LRU status instead.

4. (5) A computer has a cache, main memory, and a disk. If a reference to the cache is a hit, it takes 5 ns to retrieve the data. If a reference misses in the cache, it takes 60 ns to fetch the item from memory and put it in the cache, at which point the request is reissued to the cache. If the required item is not in main memory, it takes 9 ms to fetch the word from the disk, followed by 70 ns to copy the word to the cache, and then the reference is reissued to the cache. The cache hit ratio is .95 and the main memory hit ratio is .75. Write down the equation you would use to calculate the average time in nanoseconds to access a data item on this system.

5. (5) Explain the principle of Locality and why it is important.

6. (5) Explain the difference between serial and parallel I/O, and when one is preferred over the other.

7. (5) Describe DMA and outline what problems be considered when using DMA in a system with a cache.

8. (5) Caches can be either Virtually Addressed or Physically Addressed. Explain the difference, and give one advantage and one disadvantage to using Physically addressed caches.

9. (6) Given a logical 19-bit address and a 1024-byte physical memory for a byte-addressable machine,

How big is the physical address space?

How big is the virtual address space?

Assuming 16K-byte pages, how many page frames are there? How many pages?

Assuming .5K-byte pages, how many page frames are there? How many pages?

10. (12 pts) Here is a 12-bit Error Correction code format (same one used in class):

 $d_8 \hspace{0.1in} d_7 \hspace{0.1in} d_6 \hspace{0.1in} d_5 \hspace{0.1in} C_4 \hspace{0.1in} d_4 \hspace{0.1in} d_3 \hspace{0.1in} d_2 \hspace{0.1in} C_3 \hspace{0.1in} d_1 \hspace{0.1in} C_2 \hspace{0.1in} C_1$

a. Given the *data* bit pattern

10110110

in a machine using the above ECC code, what bit pattern gets sent to memory? (No credit will be given without work being shown.)

b. In this same machine, the following bit pattern is retrieved from memory:

$0\,0\,1\,0\,1\,1\,0\,1\,1\,0\,0\,1$

Assuming the above Error Correction code format, identify and correct any errors that may have occurred during transmission or storage. (No credit will be given without work being shown.)

11. (10 pts) What is the maximum clock frequency possible for the following circuit? (In other words, what is the maximum clock frequency that will still guarantee correct behavior?) Use the following delay values, and assume all input signals become valid at time 0:

AND: 4ns NAND: 3ns NOT: 2ns MUX: 6ns Tprop: 8ns Tsetup: 2ns Thold: 1ns



12. (5 pts) Add arrows to the following diagram to indicate which signal transitions **cause** other transitions to occur.



Now explain in words (briefly) what the arrows you have added are doing. (What is the sequence of events in words?)

- 13. (10 pts) Add the connections to the following diagram necessary to create a 12Kx16 memory. (This might be done in a machine with memory-mapped I/O, for example.) Not all of the hardware shown is required to perform this task.
 - CS Chip Select
 - OE Output Enable
 - RD Read (Read/Write, technically)



14. (15) "Flaming Ball of Burning Hydrogen" Microsystems features the "Sparkler", a byteaddressable computer with a 16-bit word size and 256 bytes of memory. In this machine accessing main memory takes 6 clock cycles (in addition to the time necessary to do a cache lookup), and the bus between main memory and the processor is 8-bits wide. In order to improve performance, they are considering adding a 32-byte physically addressed Direct-Mapped cache with a line size of 1 word and an access time of 1 cycle. Given the following address reference sequence (in Hex):

0x35,0x36,0x37,0xC3,0x34

a) Write down how you are partitioning each address (which bits are the Tag, offset, etc.)

b) In the table below, fill in the proposed Cache's Tag values after each memory reference has been processed. If it is a hit, mark the entry number to indicate this, and if it is a miss enter what the new tag should be. (X indicates the entry is invalid). There may be more Tag Array entries than you need.

Tag Array	Contents of Tag Array after processing address (Time ->)								
Entry	Initial	0x35	0x36	0x37	0xC3	0x34			
Number	Contents	(00110101)	(00110110)	(00110111)	(11000011)	(00110100)			
0	X								
1	X								
2	X								
3	X								
4	X								
5	X								
6	X								
7	X								
8	X								
9	X								
10	X								
11	X								
12	X								
13	X								
14	X								
15	X								

What is the Average Memory access time for this sequence of references?

Data Array	Data Array Contents after processing address
Entry Number	0x35
0	
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
13	
14	
15	

Now fill in the contents of the Data array after processing the given address reference. Write down only the ones that change.

Memory Contents at Hex Address XY																
Most Signifi cant		Least Signifi cant Digit (Y)														
Digit (X)	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
0	23	20	6d	61	74	74	27	73	20	67	76	69	65	77	20	73
1	68	65	6c	6c	20	73	63	72	69	70	74	0a	73	65	74	20
2	67	66	69	6c	65	20	3d	20	24	31	0a	09	65	63	68	6f
3	20	2d	6e	20	22	67	67	72	61	70	68	20	24	67	66	69
4	6c	65	2e	2e	2e	22	20	0a	09	65	63	68	6f	20	22	2e
5	73	70	20	32	22	20	3e	21	20	2f	74	6d	70	2f	74	65
6	6d	70	24	24	2e	6e	72	0a	09	65	63	68	6f	20	22	2e
7	70	6f	20	2b	30	2e	35	69	22	20	3e	3e	20	2f	74	6d
8	23	7b	92	08	22	41	85	32	69	73	11	35	97	54	31	48
9	88	73	48	72	98	21	42	85	62	65	90	84	31	56	55	83
a	43	64	84	36	59	3c	8a	95	3b	8f	0e	41	7a	40	2b	3c
b	4c	d4	c7	82	a0	38	f9	c6	29	a3	d0	9c	7d	41	2b	75
c	54	69	9c	3b	b0	2a	d9	3e	45	72	6e	f0	f9	3f	a0	0a
d	60	89	43	d8	c 0	e7	49	76	59	21	2c	c8	a8	f2	87	43
e	76	8f	2e	a9	ff	38	ae	65	dd	cf	21	84	ce	e4	34	51
f	8a	65	30	2f	c9	3a	58	72	3e	a0	4f	38	96	47	21	80

15. (15) "Flaming" decided to experiment with using a smaller, 24-byte 3-way Set Associative Cache (instead of the Direct-mapped Cache) with a line size of 1 word. Remember, the Sparkler is a byte-addressable machine with a 16-bit word size, an 8-bit bus between processor and memory, and a Main Memory access time of 6 cycles (in addition to the time necessary to to a cache lookup). The Cache access time is still 1 cycle. Given the same address reference sequence (in Hex) as before:

0x35,0x36,0x37,0xC3,0x34

a) Write down how you are partitioning each address (which bits are the Tag, offset, etc.)

b) In the table below, fi ll in the proposed Cache's Tag values after each memory reference has been processed. If it is a hit, put an "H" in the tag fi eld, and if it is a miss write down what the new tag should be. Use an LRU replacement scheme, and after each address is processed be sure to indicate the age of the references. There may be more entries than you need. MRU = Most Recently Used, LRU = Least Recently Used.

Tag Array			Contents of Tag Array after processing address (Time ->)										
Set	Entry	Initial	contents	0x35		0x36		0x37		0xC3		0x	34
#	#			(0011	0101)	(0011	0110)	(0011	0111)	(11000011)		(00110100)	
		Age	Tag	Age	Tag	Age	Tag	Age	Tag	Age	Tag	Age	Tag
	0	MRU	01100										
0	1	LRU	01110										
	2		11000										
	0		00100										
1	1	MRU	00001										
	2	LRU	01101										
	0	LRU	00100										
2	1		01001										
	2	MRU	00110										
	0	LRU	10010										
3	1		00111										
	2	MRU	10110										

What is the Average Memory access time for this sequence of references?

16. (9 pts) The following tables contain some of the information about a segmented, paged virtual memory system and certain select memory locations. Total physical memory size is 16K bytes, and the page size is 512 bytes. All numbers in this table are in Hex unless otherwise noted.

Segment Table								
Entry	Presence	Page						
Number	Bit	Table						
0	1	5						
1	0	0						
2	1	0						
3	1	7						
4	1	2						
5	1	3						
6	1	1						
7	1	4						

Page Table 0								
Entry	Present?	Disk	Frame					
Number	(1=Yes)	Addr	Number					
0	1	1234123	0x4					
1	0	0893748	0x7					
2	1	2489567	0x1					
3	1	9623873	0x5					
7	1	B0F6BD3	0x2					
10	0	32829AA	0x1					
12	1	56D87AC	0x0					
15	1	10A876D	0x6					

/		1	- T					
	Mon	2022						
wiemory								
Address		Co	ontents					
0x00A4		()x76					
0x01A4		()x73					
0x02A4		()x32					
0x03A4		()x46					
0x14A4		()x30					
0x2AA4		()x29					
0x05A4		()xa9					
0x09A4		()x74					
0x1AA4		()x05					
0x0CA4		()x23					
0x0DA4		C)xE3					
0x17A4		0	xAE					
0x26A4		()x92					

Page Table 5								
Entry	Present?	Disk	Frame					
Number	(1=Yes)	Addr	Number					
0	1	1234123	0x2					
1	0	0893748	0x3					
5	0	2489567	0x4					
7	1	9623873	0x4					
11	1	AE76BD3	0x6					
13	0	328759A	0x7					
14	1	11D87BE	0x1					
15	1	91C875D	0x2					

Page Table 2								
Entry	Present?	Disk	Frame					
Number	(1=Yes)	Addr	Number					
0	1	1234123	0x1					
1	0	0893748	0x3					
2	1	2489567	0x5					
3	1	9623873	0x7					
4	1	BC56BD3	0x9					
5	0	832759E	0x2					
11	1	46B37AC	0x4					
15	1	810476D	0x6					

Page Table 7								
Entry	Present?	Disk	Frame					
Number	(1=Yes)	Addr	Number					
0	1	1234123	0x5					
1	0	0893748	0x6					
2	1	2489567	0x1					
3	1	9623873	0x2					
4	1	AE76BD3	0x4					
5	0	328759A	0x2					
6	1	56D87AC	0x5					
7	1	10A876D	0x6					

For each of the following convert the virtual address into a physical address (if possible) and write down the value of the memory location corresponding to the address. If it is not possible to do so, explain why.

0x82A4 (**1 0 0 0 0 0 1 0 1 0 1 0 1 0 0 i** m binary).

0x5EA4 (**0 1 0 1 1 1 1 0 1 0 1 0 0 1 0 0** in binary).

0x28A4 (**0 0 1 0 1 0 0 0 1 0 1 0 0 1 0 0** in binary).

Present	Next	Output		
State	X=0	X=1	X=0	X=1
(Y1 Y2 Y3)	(Y1' Y2' Y3')	(Y1' Y2' Y3')		
000	111	011	0	0
010	101	001	0	0
011	100	000	0	1
100	001	001	0	0
101	001	001	1	1
110	100	000	0	1
111	100	000	1	1

16. (16) Given the following table, draw the Karnaugh maps for Y1', Y2', and Y3' and Z in terms of X, Y1, Y2 and Y3, and then write **minimum** boolean equations for each.













17. (10 pts) Given the following Karnaugh maps, implement the sequential machine using a JK FF for Y1, an SR FF for Y2, and a T FF for Y3. You do not need to draw the gates, but you do need to write down the **minimized** input equations for each of the inputs of each of the Flip Flops in the circuit.

