

1. (10 pts) **We're going to play Final (exam) Jeopardy!** Associate the following answers with the appropriate question. (You are given the "answers": Pick the "question" that goes best with each "answer".) The first one has been done for you.

"Answers:"

- z. Anywhere but here. v
- 1a. Memory that does not go away when the power is turned off.
- 1b. A small fast memory holding recently accessed data and/or instructions.
- 1c. A technique used in CD-ROM Drives to increase storage density.
- 1d. The ability of an I/O device to write directly into memory.
- 1e. A binary digit appended to a group of binary digits to make the sum of all the digits an even number.
- 1f. A setup that requires the use of a clock.
- 1g. A type of memory that uses capacitors to store data.
- 1h. A structure that holds recent mappings of virtual to physical addresses.
- 1i. A Flip Flop.
- 1j. One penny.

"Questions:"

- a) What is synchronous timing?
- b) What is asynchronous timing?
- c) What is a circuit that exhibits purely sequential behavior?
- d) What is an Even Parity bit?
- e) What is an Odd Parity bit?
- f) How much did Professor Farrens spend on 200 burnable CD's?
- g) What is a Cache?
- h) What is DMA?
- i) What is an Address Translation Lookaside Buffer (or TLB)?
- j) What is an interrupt?
- k) What is the goal of the Memory Hierarchy?
- l) What is a Page?
- m) What is a Page Fault?
- n) What is Volatile memory?
- o) What is Non-Volatile memory?
- p) What is Constant Linear Velocity?
- q) What is Constant Angular Velocity?
- r) What is the goal of multiprogramming?
- s) What is Static RAM?
- t) What is Dynamic RAM?
- v) Where would I rather be right now than where I am?

4. (4) A computer has a cache, main memory, and a disk. If a reference to the cache is a hit, it takes 3 ns to retrieve the data. If a reference misses in the cache, it takes 90 ns to fetch the item from memory and put it in the cache, at which point the request is reissued to the cache. If the required item is not in main memory, it takes 14 ms to fetch the word from the disk, followed by 90 ns to copy the word to the cache, and then the reference is reissued to the cache. The cache hit ratio is .93 and the main memory hit ratio is .83. Write down the equation you would use to calculate the average time in nanoseconds to access a data item on this system.
5. (5) What is the goal of the memory heirarchy? What principle makes it possible to achieve this goal? Give the two types, and explain what they are.

9. (4) Given a logical 25-bit address and a 2Meg (2048K)-byte physical memory for a byte-addressable machine,

How big is the physical address space? 2^{21}

How big is the virtual address space? 2^{25}

Assuming 64K-byte pages, how many page frames are there? How many pages? How many bits wide is the page table?

32 page frames, 512 pages, 5 bits wide

Assuming 1K-byte pages, how many page frames are there? How many pages? How many bits wide is the page table?

2^{11} frames, 2^{15} pages, 11 bits wide

10. (10 pts) Here is a 12-bit Error Correction code format (same one used in class):

$d_8 \ d_7 \ d_6 \ d_5 \ C_4 \ d_4 \ d_3 \ d_2 \ C_3 \ d_1 \ C_2 \ C_1$

- a. Given the *data* bit pattern

0 0 0 1 0 1 0 1

in a machine using the above ECC code, what bit pattern gets sent to memory? (No credit will be given without work being shown.)

- b. In this same machine, the following bit pattern is retrieved from memory:

0 1 0 1 1 0 1 0 1 1 1 0

Assuming the above Error Correction code format, identify and correct any errors that may have occurred during transmission or storage. (No credit will be given without work being shown.)


11. (10 pts) What is the maximum clock frequency possible for the following circuit? (In other words, what is the maximum clock frequency that will still guarantee correct behavior?) Use the following delay values, and assume all input signals become valid at time 0:

AND: 4ns NAND: 3ns NOT: 2ns MUX: 5ns

Tprop (TFF): 7ns Tsetup (TFF): 3ns Thold (TFF): 1ns


Tprop (DFF): 8ns Tsetup (DFF): 3ns Thold (DFF): 1ns

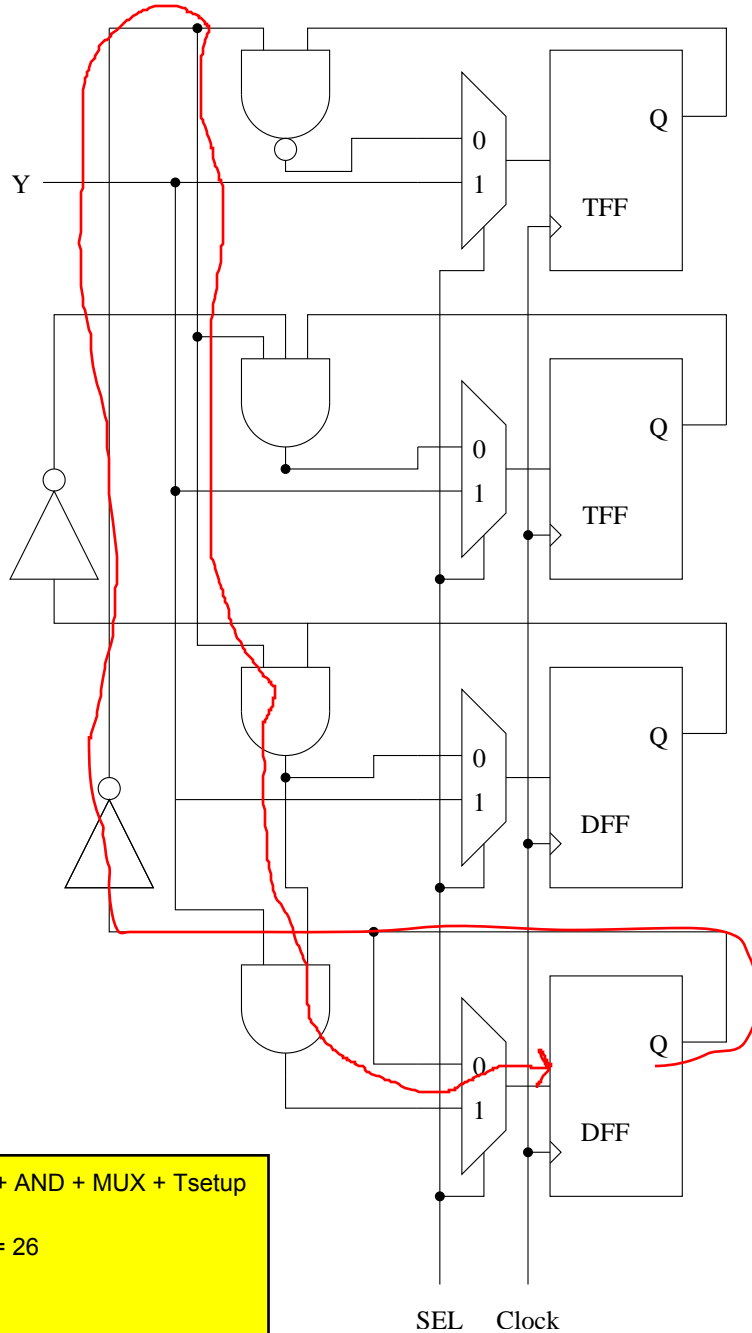Note: You must show the path in order to get credit.



$T_{prop} + NOT + AND + AND + MUX + T_{setup}$
 $8 + 2 + 4 + 4 + 5 + 3 = 26$
 Freq = $1/26ns$

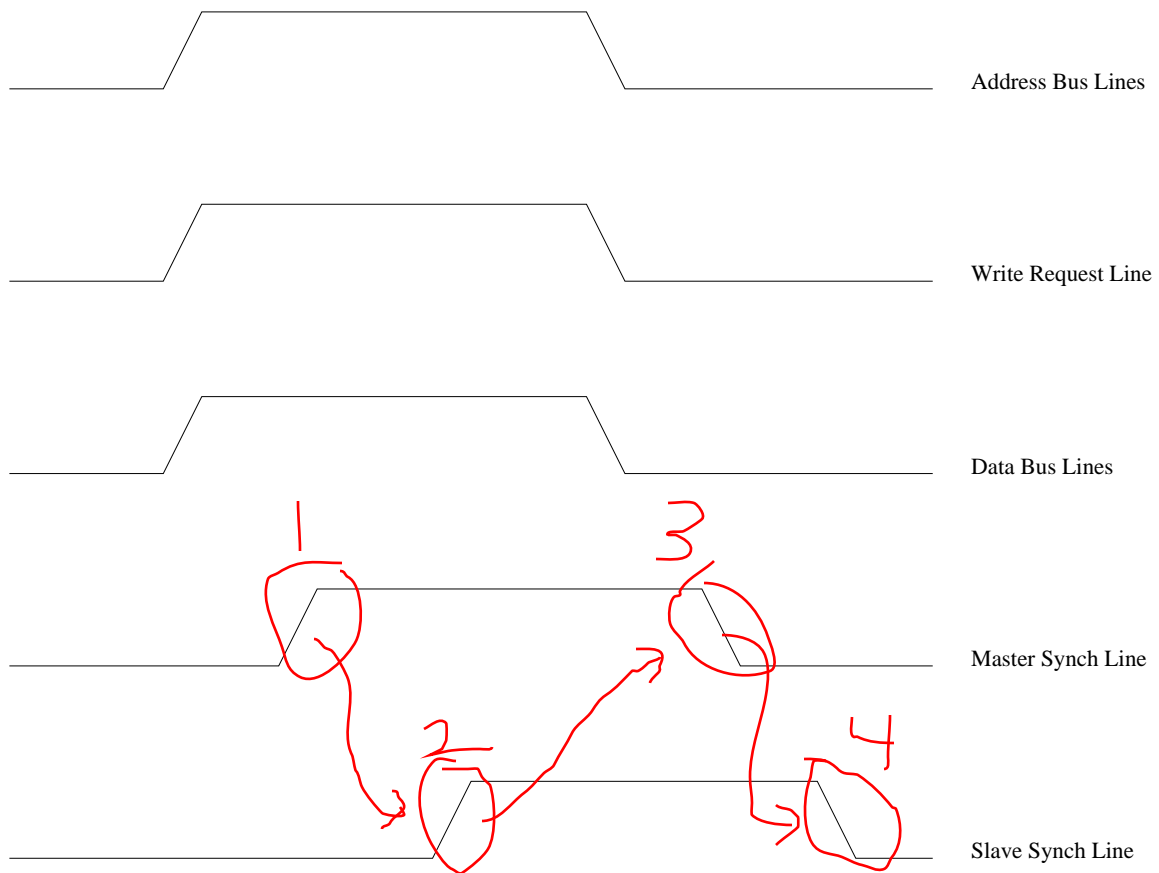12. (5 pts) Add arrows to the following diagram to indicate which signal transitions **cause** other transitions to occur.




Now explain in words (briefly) what the arrows you have added are doing. (What is the sequence of events in words?)

1. Please perform the requested action specified on the control lines, Slave.
2. I have done what you asked, Master.
3. Thank you for performing that task for me!
4. You are most welcome - I was happy to do it, and will be glad to do it again in the future if you desire more assistance. Now, I am going to return to my slave quarters to await further commands from you, Master.

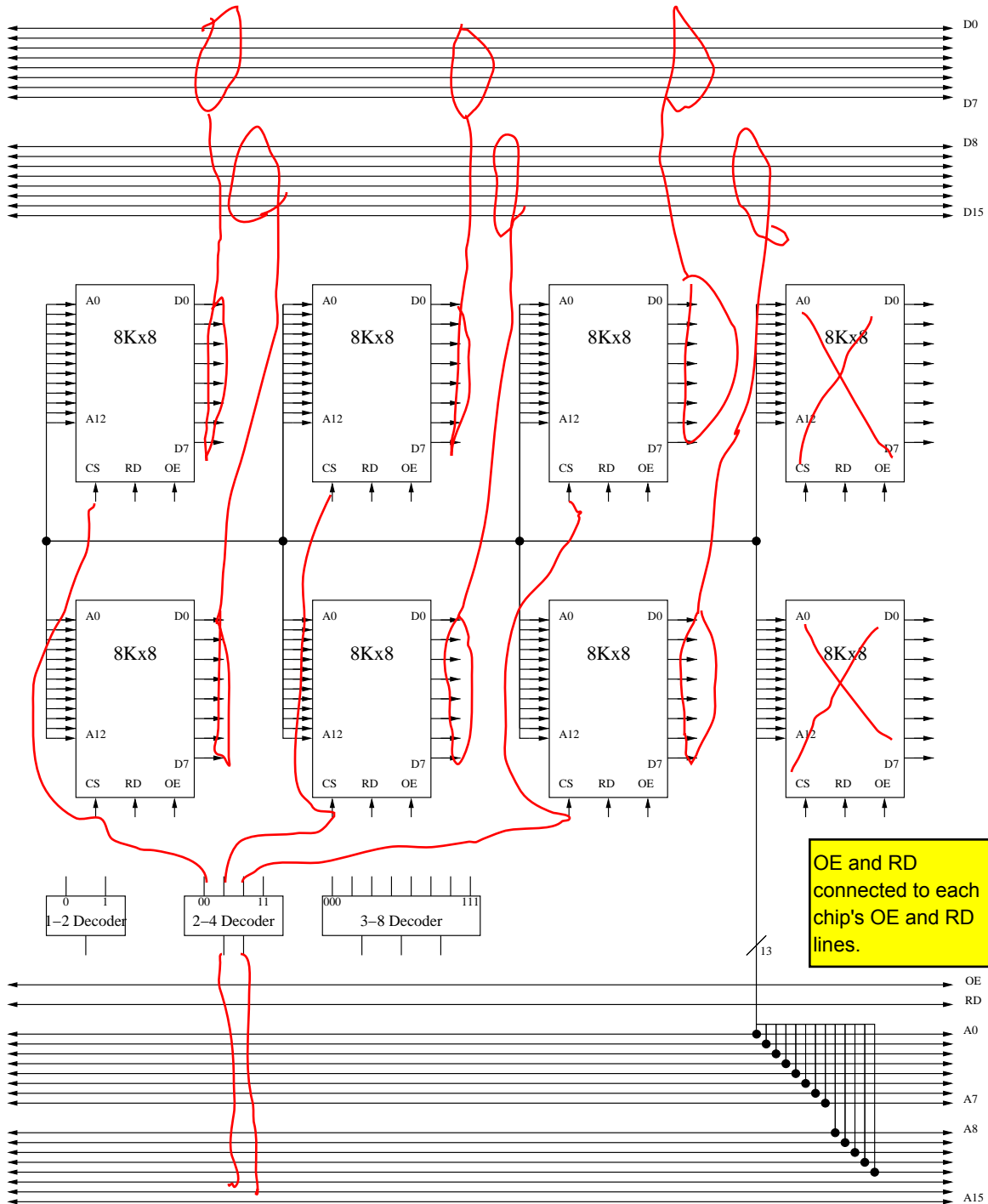13. (10 pts) Add the connections to the following diagram necessary to create a 24Kx16 memory. (This might be done in a machine with memory-mapped I/O, for example.) Not all of the hardware shown is required to perform this task.

CS - Chip Select
 OE - Output Enable
 RD - Read (Read/Write, technically)



14. (17) Hemlock Pickers Computer Corporation features the "Smoothie", a byte-addressable computer with a 64-bit word size and 256 bytes of memory. In this machine accessing main memory takes 5 clock cycles (in addition to the time necessary to do a cache lookup), and the bus between main memory and the processor is 8-bits wide. In order to improve performance, they are considering adding a 64-byte physically addressed Direct-Mapped cache with a line size of 1 word and an access time of 1 cycle. Given the following address reference sequence (in Hex):

0xB5,0x36,0x37,0xCB,0x34

- a) Write down how you are partitioning each address (which bits are the Tag, offset, etc.)

Left most 2 are tag, middle 3 are entry number, right most 3 indicate offset into line.

- b) In the table below, fill in the proposed Cache's Tag values after each memory reference has been processed. If it is a hit, mark the entry number to indicate this, and if it is a miss enter what the new tag should be. (X indicates the entry is invalid). There may be more Tag Array entries than you need.

Tag Array Entry Number	Contents of Tag Array after processing address (Time ->)					
	Initial Contents	0xB5 (10110101)	0x36 (00110110)	0x37 (00110111)	0xCB (11001011)	0x34 (00110100)
0	X					
1	X				M 11	
2	X					
3	X					
4	X					
5	X					
6	X	M 10	M 00	H		H
7	X					
8	X					
9	X					
10	X					
11	X					
12	X					
13	X					
14	X					
15	X					

What is the Average Memory access time for this sequence of references?

25 ns (125/5)

Now fill in the contents of the Data array after processing the given address reference. Write down only the ones that change.

Data Array	Data Array Contents after processing address
Entry Number	0xB5
0	
1	
2	
3	
4	
5	
6	4c d4 c7 82 a0 38 f9 c6
7	
8	
9	
10	
11	
12	
13	
14	
15	

Memory Contents at Hex Address XY																
Most Significant Digit (X)	Least Significant Digit (Y)															
	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
0	23	20	6d	61	74	74	27	73	20	67	76	69	65	77	20	73
1	68	65	6c	6c	20	73	63	72	69	70	74	0a	73	65	74	20
2	67	66	69	6c	65	20	3d	20	24	31	0a	09	65	63	68	6f
3	20	2d	6e	20	22	67	67	72	61	70	68	20	24	67	66	69
4	6c	65	2e	2e	2e	22	20	0a	09	65	63	68	6f	20	22	2e
5	73	70	20	32	22	20	3e	21	20	2f	74	6d	70	2f	74	65
6	6d	70	24	24	2e	6e	72	0a	09	65	63	68	6f	20	22	2e
7	70	6f	20	2b	30	2e	35	69	22	20	3e	3e	20	2f	74	6d
8	23	7b	92	08	22	41	85	32	69	73	11	35	97	54	31	48
9	88	73	48	72	98	21	42	85	62	65	90	84	31	56	55	83
a	43	64	84	36	59	3c	8a	95	3b	8f	0e	41	7a	40	2b	3c
b	4c	d4	c7	82	a0	38	f9	c6	29	a3	d0	9c	7d	41	2b	75
c	54	69	9c	3b	b0	2a	d9	3e	45	72	6e	f0	f9	3f	a0	0a
d	60	89	43	d8	c0	e7	49	76	59	21	2c	c8	a8	f2	87	43
e	76	8f	2e	a9	ff	38	ae	65	dd	cf	21	84	ce	e4	34	51
f	8a	65	30	2f	c9	3a	58	72	3e	a0	4f	38	96	47	21	80

15. (15) Hemlock Pickers decided to experiment with using a smaller, 48-byte 3-way Set Associative Cache (instead of the Direct-mapped Cache) with a line size of 1 word. Remember, the Smoothie is a byte-addressable machine with a 64-bit word size, an 8-bit bus between processor and memory, and a Main Memory access time of 5 cycles (in addition to the time necessary to to a cache lookup). The Cache access time is still 1 cycle. Given the same address reference sequence (in Hex) as before:

0xB5,0x36,0x37,0xCB,0x34

- a) Write down how you are partitioning each address (which bits are the Tag, offset, etc.)

Left most 4 bits are tag, next bit is entry number, right most 3 are offset into line

- b) In the table below, fill in the proposed Cache's Tag values after each memory reference has been processed. If it is a hit, put an "H" in the tag field, and if it is a miss write down what the new tag should be. Use an LRU replacement scheme, and after each address is processed be sure to indicate the age of the references. There may be more entries than you need. MRU = Most Recently Used, LRU = Least Recently Used.

Tag Array				Contents of Tag Array after processing address (Time ->)									
Set #	Entry #	Initial contents		0xB5 (10110101)		0x36 (00110110)		0x37 (00110111)		0xCB (11001011)		0x34 (00110100)	
		Age	Tag	Age	Tag	Age	Tag	Age	Tag	Age	Tag	Age	Tag
0	0	MRU	1100			LRU		LRU				LRU	
	1	LRU	1110	MRU	1011								
	2		1000	LRU		MRU	0011	MRU	H			MRU	H
1	0		0100							LRU			
	1	MRU	0001										
	2	LRU	1100							MRU	H (1100)		
2	0	LRU	0100										
	1		1001										
	2	MRU	0110										
3	0	LRU	0010										
	1		0111										
	2	MRU	0110										

What is the Average Memory access time for this sequence of references?

Average memory reference time is 17 ns (85/5)

16. (6 pts) The following tables contain some of the information about a segmented, paged virtual memory system and certain select memory locations. Total physical memory size is 16K bytes, and the page size is 512 bytes. All numbers in this table are in Hex unless otherwise noted.

Segment Table		
Entry Number	Presence Bit	Page Table
0	1	5
1	0	0
2	1	0
3	1	7
4	1	2
5	1	3
6	1	1
7	1	4

Page Table 0			
Entry Number	Present? (1=Yes)	Disk Addr	Frame Number
0	1	1234123	0x4
1	0	0893748	0x7
2	1	2489567	0x1
3	1	9623873	0x5
7	1	B0F6BD3	0x2
10	0	32829AA	0x1
12	1	56D87AC	0x0
15	1	10A876D	0x6

Page Table 2			
Entry Number	Present? (1=Yes)	Disk Addr	Frame Number
0	1	1234123	0x1
1	0	0893748	0x3
2	1	2489567	0x5
3	1	9623873	0x7
4	1	BC56BD3	0x9
5	0	832759E	0x2
11	1	46B37AC	0x4
15	1	810476D	0x6

Memory	
Address	Contents
0x00A4	0x76
0x01A4	0x73
0x02A4	0x32
0x03A4	0x46
0x04A4	0x30
0x2AA4	0x29
0x05A4	0xa9
0x09A4	0x74
0x1AA4	0x05
0x0CA4	0x23
0x0DA4	0xE3
0x17A4	0xAE
0x26A4	0x92

Page Table 5			
Entry Number	Present? (1=Yes)	Disk Addr	Frame Number
0	1	1234123	0x2
1	0	0893748	0x3
5	0	2489567	0x4
7	1	9623873	0x4
11	1	AE76BD3	0x6
13	0	328759A	0x7
14	1	11D87BE	0x1
15	1	91C875D	0x2

Page Table 7			
Entry Number	Present? (1=Yes)	Disk Addr	Frame Number
0	1	1234123	0x5
1	0	0893748	0x6
2	1	2489567	0x1
3	1	9623873	0x2
4	1	AE76BD3	0x4
5	1	328759A	0x2
6	1	56D87AC	0x5
7	1	10A876D	0x6

For each of the following convert the virtual address into a physical address (if possible) and write down the value of the memory location corresponding to the address. If it is not possible to do so, explain why.

0x9EA4 (100)1111)010100100 in binary).

Seg 4, Page Table 2, entry 15, frame 6
Addr 0xCA4, Value = 0x23

0x74A4 (0111)1010)010100100 in binary).







Page Fault (Seg 3, Page table 7, entry 10)

0x3CA4 (001)1110)010100100 in binary).

Seg Fault

17. (16) Given the following table, draw the Karnaugh maps for $Y1'$, $Y2'$, and $Y3'$ and Z in terms of X , $Y1$, $Y2$ and $Y3$, and then write **minimum** boolean equations for each.

Present State (Y1 Y2 Y3)	Next State		Output	
	X=0 (Y1' Y2' Y3')	X=1 (Y1' Y2' Y3')	X=0	X=1
000	001	001	0	0
001	101	101	0	0
010	001	001	0	0
011	100	100	0	0
100	001	001	0	1
101	011	011	1	1
110	001	001	0	1

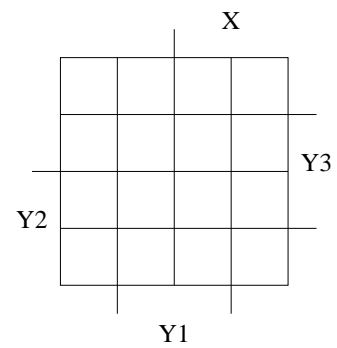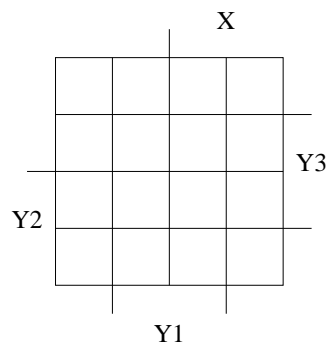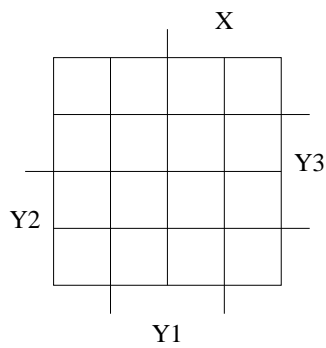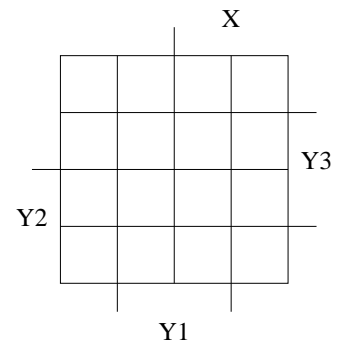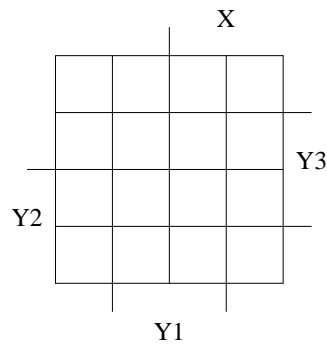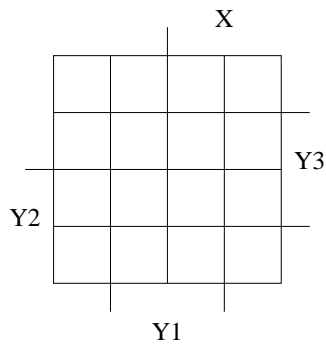

18. (15 pts) Given the following Karnaugh maps, implement the sequential machine using a JK FF for Y1, an SR FF for Y2, and a T FF for Y3. You do not need to draw the gates, but you do need to write down the **minimized** input equations for each of the inputs of each of the Flip Flops in the circuit.

